 


## Sheet # 3

### Flip Flops


1. The S and R waveforms provided in the following figure are applied to the inputs of the NOR SR latch. Write the mode of operation for each time period and draw the Q output waveform that results.




2. Repeat prob.1 when NOR gates are replaced with NAND gates.

3. Construct a gated D latch using NOR and AND gates instead of using NAND gates.

 4. The D and CLK waveforms shown are applied to the inputs of the controlled D-FF shown. Draw the Q output waveform that results.



 5. For the Master-Slave JK flip-flop shown, draw the output Q and write the mode of operation for each time period.



6. How to use the JK flip-flop as a D flip-flop and vice versa. Use any additional gates you need.

7. A set-dominate flip-flop has a set and a reset input. It differs from a conventional RS flip-flop in that an attempt to simultaneously set and reset results in setting the flip-flop.

- a) Obtain the characteristic table and characteristic equation for the set-dominate flip-flop.
- b) Obtain a logic diagram for an asynchronous set-dominate flip-flop.