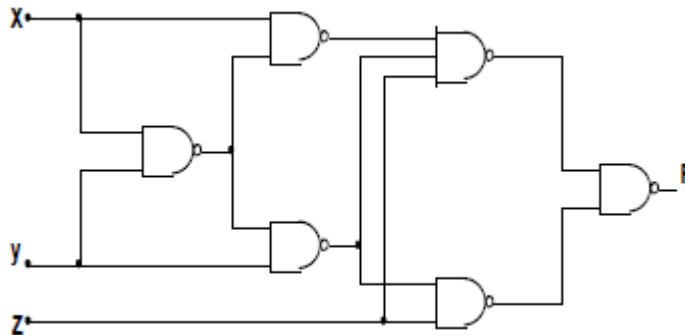


Sheet #2

Combinational Circuits

1. Obtain the truth table for the circuit shown in the figure. Draw an equivalent circuit for F with fewer NAND gates.



2. A majority function is generated in a combinational circuit in which the output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise. Design a 3-input majority function.
3. Design a comparator circuit that compares two numbers. Each number consists of two digits.
i.e. $N_1 = A_1A_0$ and $N_2 = B_1B_0$
to determine if N_1 is *greater, equal, or less* than N_2 .
4. Design a combinational circuit whose input is a 4-bit number and whose output is the two's complement of the input number.
5. Design a combinational logic circuit that converts a decimal digital from the 8421 code to BCD.
6. Design a combinational logic circuit that converts a decimal digital from the 8421 code to Gray code.
7. Design a combinational circuit that forms the binary sum of two 2-bit numbers A_1A_0 and B_1B_0 . Do not use half adders or full adders. Design the circuit starting with a truth table.
8. Design a BCD to Excess-3 code converter with 4-bit adder. What must be done to change the circuit to an Excess-3 to BCD code converter?

9. Design a binary multiplier that multiplies two 4-bit numbers. Use AND gates and binary adders.
10. Develop a 3-to-8 decoder using NOR gates only, and draw its logic diagram.
11. Construct a 5-to-32 decoder using the following decoders:
- 2-to-4 line decoder, active low outputs and a single active low enable.
 - 3-to-8 line decoder, active low outputs with 2 active low and one active high enable.
12. Construct an 8-to-1 line multiplexer with enable input.
13. A combinational circuit is defined by the following three Boolean functions. Design the circuit with a decoder and external gates.
- $$F_1 = \overline{xy} + xy\overline{z}$$
- $$F_2 = \overline{x} + y$$
- $$F_3 = xy + \overline{xy}$$
14. Repeat problem 13 using a 4-to-1 multiplexer.
15. Design an octal –to- binary priority encoder.

Best Wishes of Success