

Data Processing Circuits

Decoders


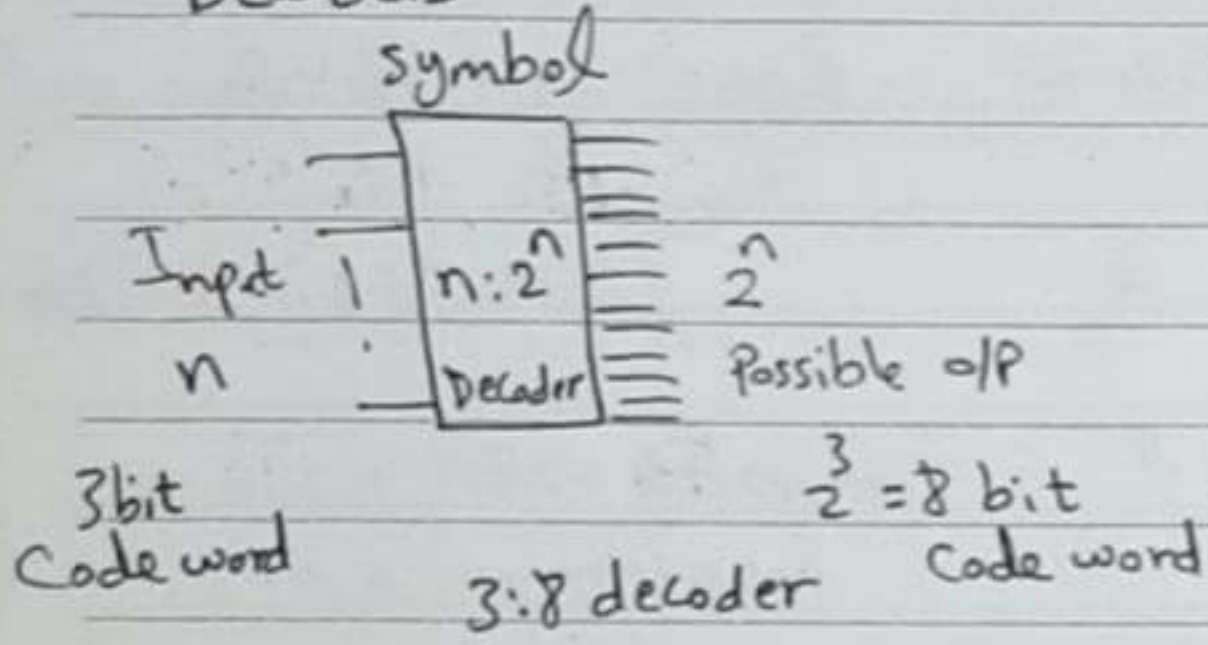


Table F<sup>n</sup> of decoder:- "Active high decoder"

A	B	C	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Active high decoder  $\rightarrow$  output  $\oplus$  corresponding to minterm of input.  
 $D_0$  corresponding to "minterm"  $\bar{A}\bar{B}\bar{C}$ .

\* Symbol of Active low:-

 


\* Realization of Multiple output function using decoder :-

Active high output 74138

$$* F = \sum m(1, 3, 5, 6)$$


$$= \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC$$

$$= m_1 + m_3 + m_5 + m_6$$

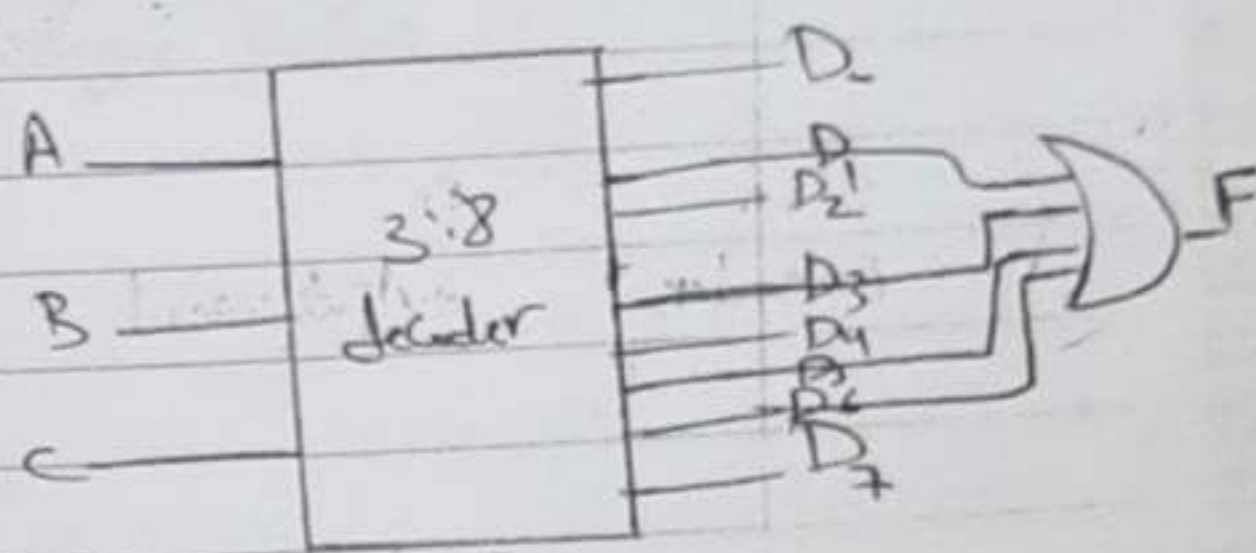

$$* F = \prod M(1, 3, 5, 6)$$
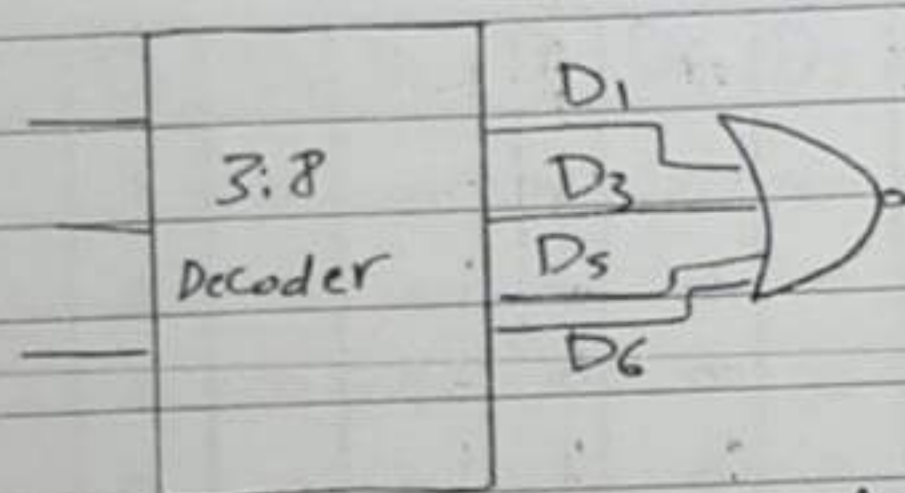
$$= (\bar{A} + \bar{B} + C) \cdot (\bar{A} + B + C) \cdot (A + \bar{B} + C) \cdot (A + B + \bar{C}) = M_1 M_3 M_5 M_6$$



$$F = (m_1 + m_3 + m_5 + m_6)$$

$$= \bar{m}_1 \cdot \bar{m}_3 \cdot \bar{m}_5 \cdot \bar{m}_6$$

$$= M_1 M_3 M_5 M_6$$

Active low decoder

$$* F = \sum m(1, 3, 5, 6)$$


$$\rightarrow = \prod M(0, 2, 4, 7)$$

$$(\bar{M}_1 M_3 M_5 M_6) =$$

$$\bar{M}_1 + \bar{M}_3 + \bar{M}_5 + \bar{M}_6$$


$$= m_1 + m_3 + m_5 + m_6$$

$$\bar{F} = \sum m(0, 2, 4, 7)$$

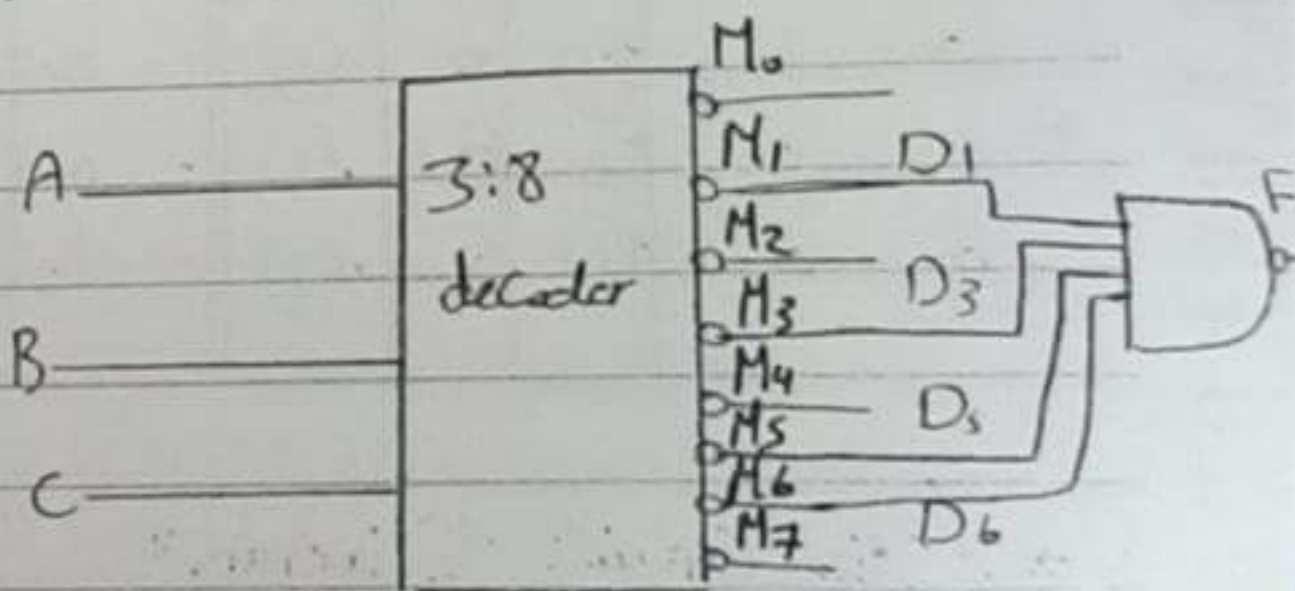

?? OR gate

$$* F = \prod M(1, 3, 5, 6)$$

 


?? AND?

0 → 9

\* B.C.D. (Binary Coded Decimal) to 7-segment

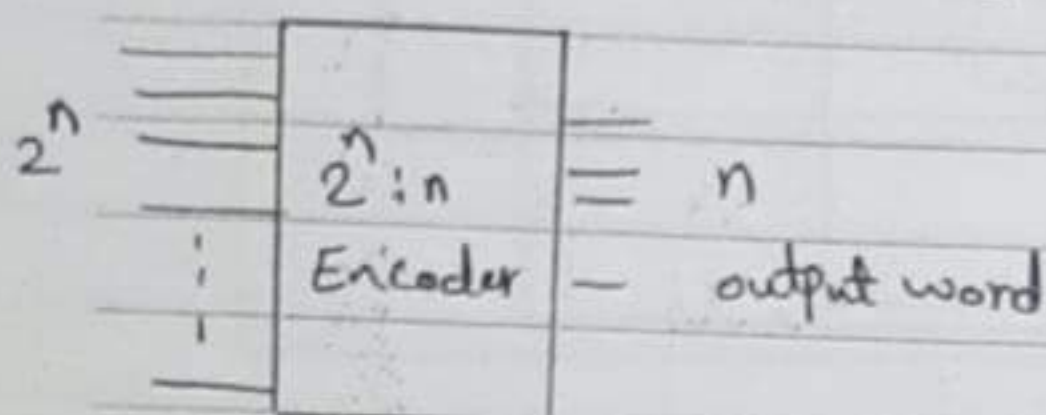\* Encoder :- Multiple i/p, Multiple o/p Combined logic Circuit.



\* Octal to Binary Encoder & 8x3 Encoder  
 "code word of length 8" to "code word of length 3"


D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

\* Logic Circuit "Diagram"

$$A = D_4 + D_5 + D_6 + D_7$$

$$B = D_2 + D_3 + D_6 + D_7$$

$$C = D_1 + D_3 + D_5 + D_7$$

 

\* حسب قيمة الأثرية أن  $D_0$  هي منوية والكل من غيرها  $\bar{A}\bar{B}\bar{C}$  (Zero) undermined output "فلا" \*

Priority encoder كالتالي \*

\* Priority encoder \* is a practical form of an encoder.

(4bit Priority encoder)

input				output		
$D_0$	$D_1$	$D_2$	$D_3$	A	B	V
0	0	0	0	*	*	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

\* 8 bit  
في الكود

$D_0, D_1$	$D_2, D_3$	01	11	10
00		11	11	11
01		11	11	11
11		11	11	11
10		11	11	11

$A = D_2 + D_3$

$D_0, D_1$	$D_2, D_3$	00	01	11	10
00		11	11		
01		11	11	11	
11		11	11	11	11
10		11	11	11	11

$B = D_3 + D_1 D_2$

	D <sub>2</sub> D <sub>3</sub>			
D <sub>1</sub>	00	01	11	10
00	0	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$V = D_2 + D_3 + D_1 + D_0$$

\* Logic Circuit of A, B, C "Priority Encoder"

