

lec 6
11/12/16

Data Processing Circuits

Decoders

symbol


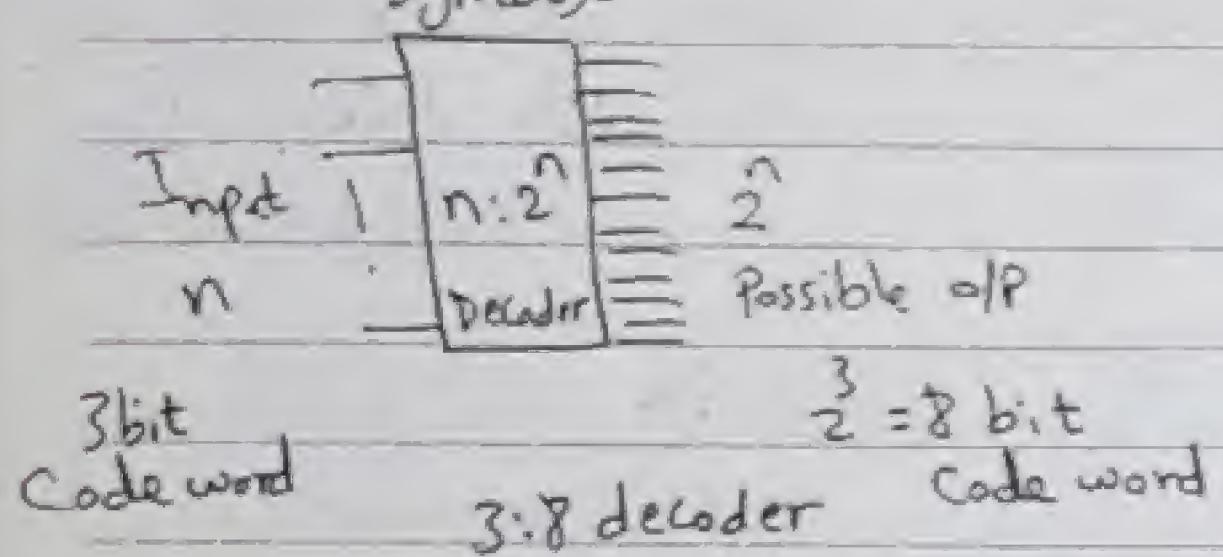


Table F of decoder:- "Active high decoder"

A	B	C	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Active high decoder \rightarrow output \Rightarrow minterm of input.
 D_0 corresponding to "minterm" $\bar{A}\bar{B}C$.

Symbol of Active low:-

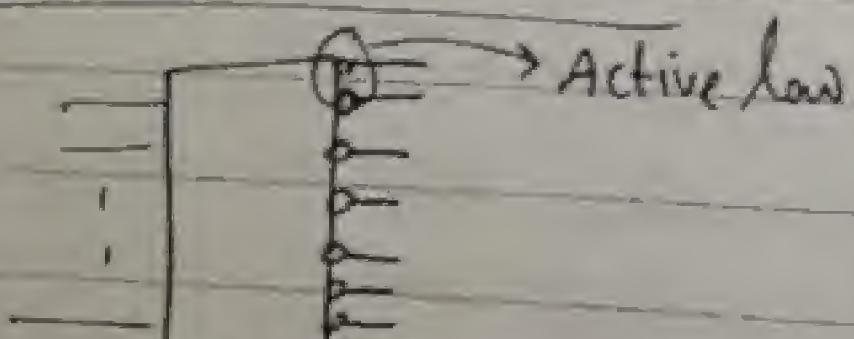


* Realization of Multiple output function using decoder -

↳ Active high output 74138

$$* F = \sum m(1, 3, 5, 6)$$


$$= \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + AB\bar{C}$$

$$= m_1 + m_3 + m_5 + m_6$$

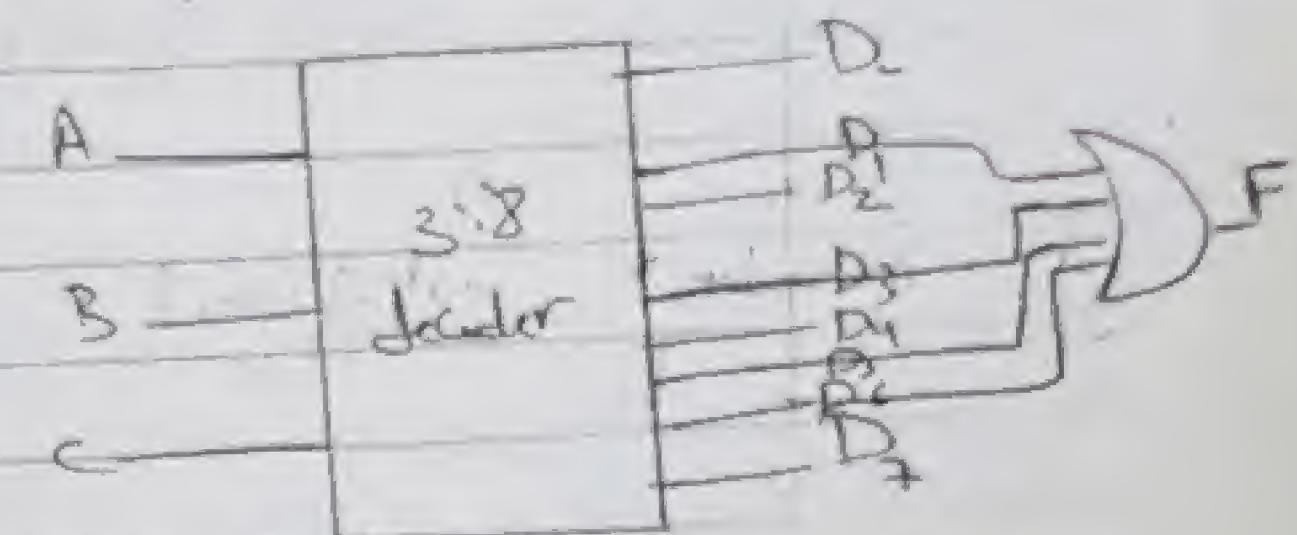

$$* F = \prod M(1, 3, 5, 6)$$
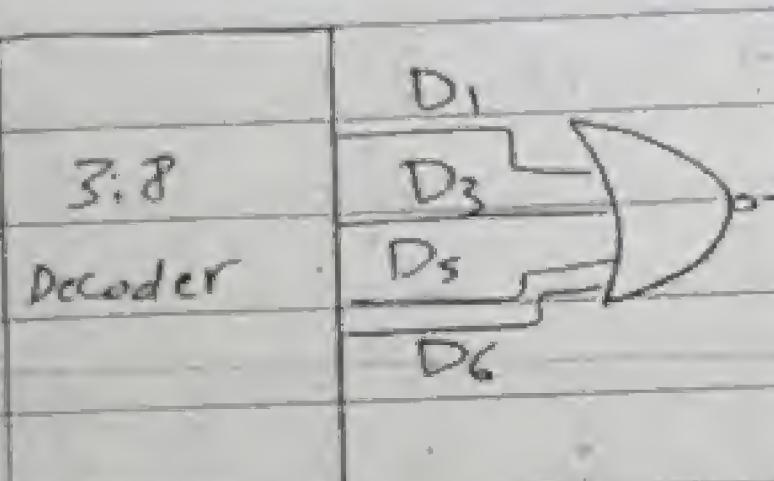
$$= (\bar{A} + \bar{B} + C) \cdot (\bar{A} + B + C) \cdot (A + \bar{B} + \bar{C}) \cdot (A + B + \bar{C}) = M_1 M_3 M_5 M_6$$



$$F = \overline{(m_1 + m_3 + m_5 + m_6)}$$

$$= \overline{m_1} \cdot \overline{m_3} \cdot \overline{m_5} \cdot \overline{m_6}$$

$$= M_1 M_3 M_5 M_6$$

Active low decoder

$$* F = \sum m(1, 3, 5, 6)$$


$$\hookrightarrow = \prod M(0, 2, 4, 7)$$

$$(M_1 M_3 M_5 M_6) =$$

$$\bar{M}_1 + \bar{M}_3 + \bar{M}_5 + \bar{M}_6$$


$$= m_1 + m_3 + m_5 + m_6$$

$$F = \sum m(0, 2, 4, 7)$$

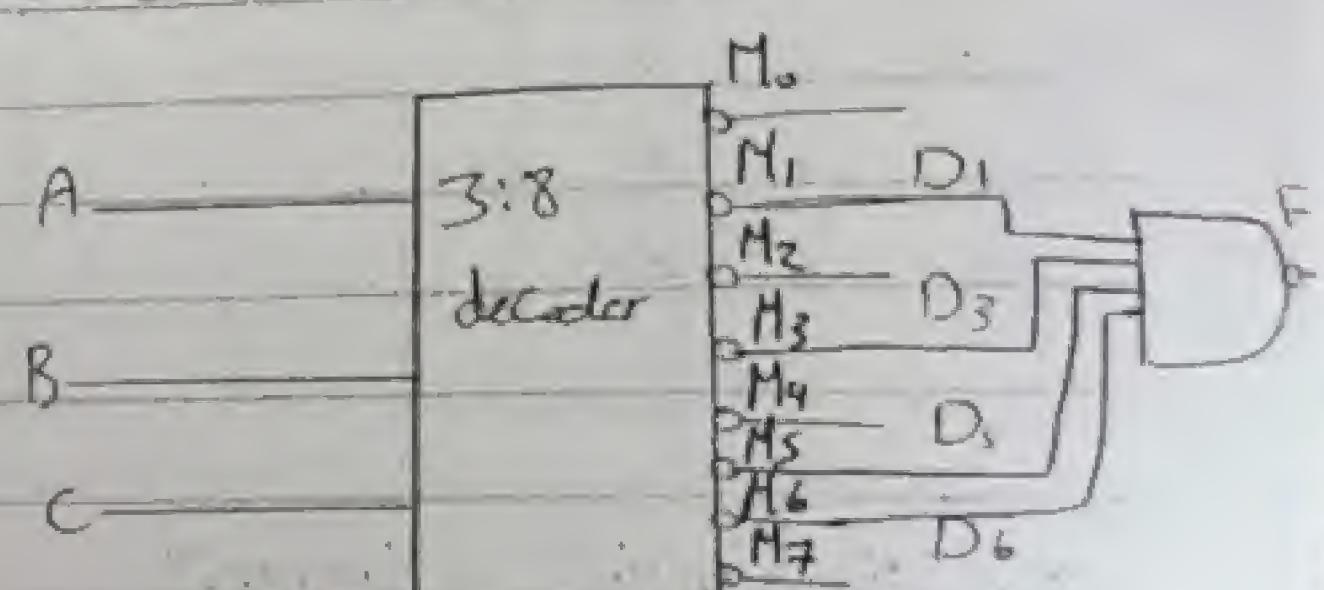

? OR (multiple solutions)

$$* F = \prod M(1, 3, 5, 6)$$

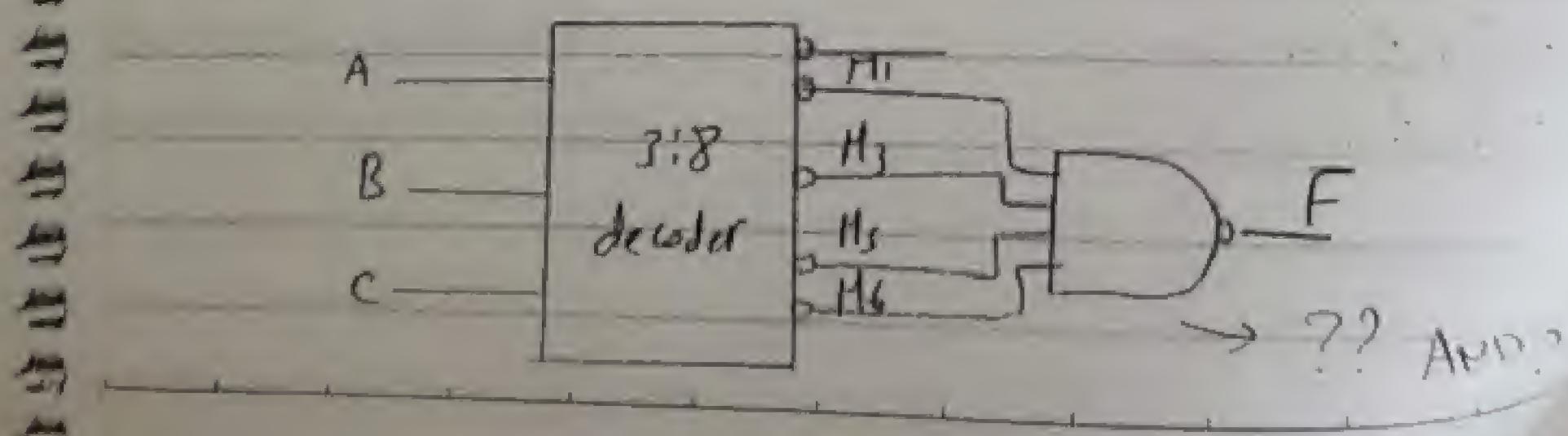


? AND?

$0 \rightarrow 9$

* BCD (Binary coded Decimal) to 7-segment.

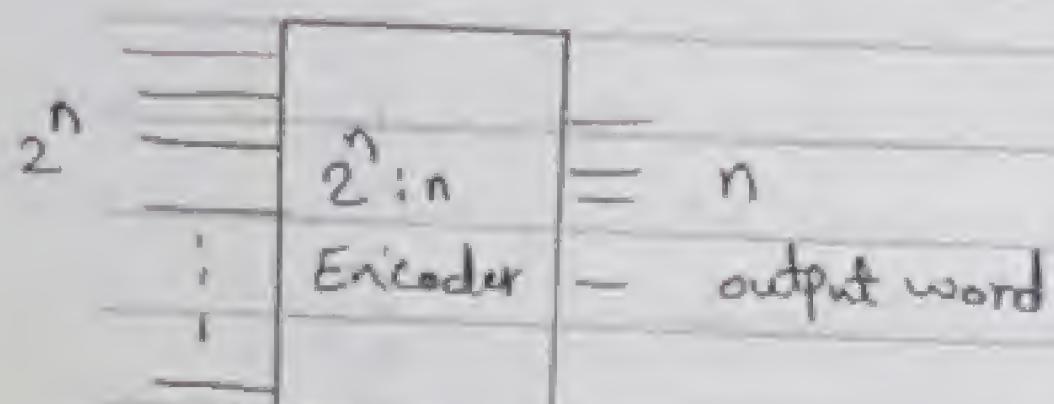* Encoder :- Multiple i/p, Multiple o/p Combinational logic circuit.



* Octal to Binary Encoder $\cong 8 \times 3$ Encoder
"Code word of length 8" to code word of length 3"


D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	0
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

* logic circuit "Diagram"

$$A = D_4 + D_5 + D_6 + D_7$$

$$B = D_2 + D_3 + D_6 + D_7$$

$$C = D_1 + D_3 + D_5 + D_7$$

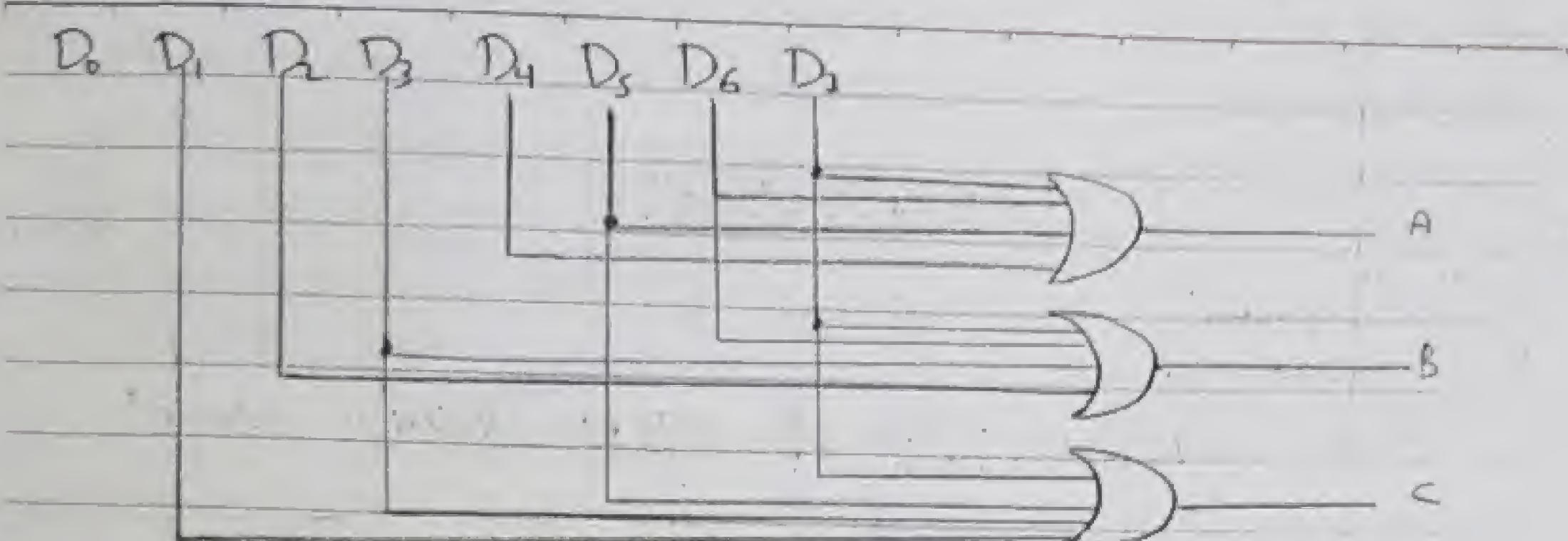

(200) $\bar{A}\bar{B}\bar{C}$ میں اے وڈا لے، اسے جیسے دیجیتال ایڈج پر
undetermined output "X" کو "2" کا دلواہ دیا جائے گا
Priority encoder جیکے اسے جو *

* Priority encoder → is a practical form of an encoder

(4bit Priority encoder)

Input				Output			→ 8 bit	out
D ₀	D ₁	D ₂	D ₃	A	B	V		
0	0	0	0	*	*	0		
1	0	0	0	0	0	1		
X	1	0	0	0	1	1		
X	X	1	0	1	0	1		
X	X	X	1	1	1	1		

D ₀	D ₁	D ₂	D ₃
00	1	1	1
01	1	1	1
11	1	1	1
10	1	1	1

$$A = D_2 + D_3$$

$$B = D_3 + D_1 \bar{D}_2$$

D ₀	D ₁	D ₂	D ₃
00	1	1	1
01	1	1	1
11	1	1	1
10	1	1	1

D_2/D_3	00	01	11	10
00	1	0	1	0
01	0	1	0	1
11	1	1	1	1
10	1	1	0	0

$$V = D_2 + D_3 + D_1 + D_0$$

+ logic circuit of A, B, C "Priority encoder"

