

## RC Timers and Timing Circuits

Timers and timing circuits are used in a wide variety of applications from short time delays of a few nanoseconds used in digital circuitry and computers to long periods of thousands of hours used to control daily, weekly, or yearly events. Electronic circuits can provide this function reliably, accurately, and repeatably, with no need for any user input or monitoring once the time has been set.

While most timers used for everyday applications in consumer goods are now implemented with or are part of a microcontroller system, for simple applications this is not always necessary. The use of a simple circuit based on a 555-type timer or a multivibrator may be more appropriate in these cases. Where high accuracy is needed, a crystal oscillator and a divider chain can be used.

There are a number of CMOS logic chips useful for this purpose. R-C (resistor-capacitor) or L-C circuits are useful where timing errors of a few percent are acceptable, but where accurate timing is a must crystal oscillators or other circuits with stable resonators should be used. The oscillator circuit is often

referred to as the clock, since it generates time intervals that are counted in some way to produce the desired timing interval.

However, the simplest timers are based on the charging and discharging of a capacitor through a resistor or current source. This approach has been around for a long time, even though its accuracy is somewhat limited (1–10 percent). We will confine this discussion to timers using RC components as timing elements. First, a few basic concepts.

### The Basics

The voltage across a capacitor is equal to the charge on it divided by the capacitance, in any consistent system of units. Charge is usually measured in Coulombs and capacitance in Farads. Current is defined as a flow of charge. The Ampere, or unit of current, is defined as that current produced by one coulomb of charge flowing across a given surface in one second. A one-ohm resistor will show a one-volt drop across it with one ampere (or one coulomb per second) flowing through it. In a practical situation, the presence of one ampere of current in a wire signifies that one coulomb

of charge flows past a given point in one second. A one-farad capacitor will have a charge of one coulomb when there is one volt of potential difference between the plates. If we connect a one-ampere current source across a one-farad capacitor, the voltage across it will rise at the rate of one volt per second, continuing to rise at this rate as long as the charging current remains constant. By knowing the current and the capacitance, we can accurately predict how long it will take to reach a certain voltage. This voltage may be that needed to produce some desired action. Conversely, if we know the capacitance, final voltage needed to produce that action, and the time delay desired, we can calculate the necessary charging current. This can be used as a basis for a timer circuit.

However, the problem in real life is that one-farad capacitors and ideal one-ampere current sources are not very practical to use. One-farad capacitors are usually of the memory-backup type limited to low voltages used in logic circuitry, and units rated at 15 volts or so are physically very large and expensive. One-ampere current sources involve extra electronic circuitry and are limited


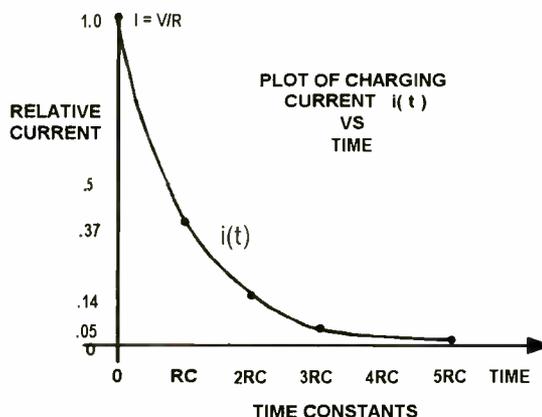
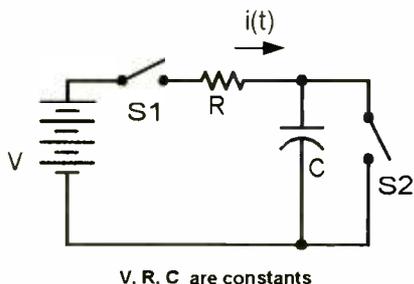


FIG 1 R-C CHARGING CIRCUIT

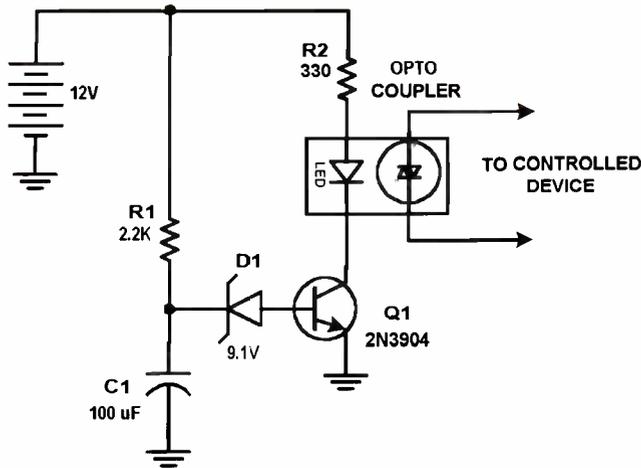

THIS CIRCUIT PRODUCES A DELAY IN TURNING ON THE OPTOCOUPLER USING COMPONENTS R1, C1, D1, AND Q1

FIG 2 SIMPLE TIMER CIRCUIT

as to output voltages they can achieve and still maintain one-ampere current flow. This, at best, would be a few hundred volts and, practically speaking, could be dangerous to work with. Much smaller capacitors of a few microfarads or less and much lower charging currents are used in practice. This allows use of standard-size electronic components. It is not necessary to use an ideal current source either. A voltage with a series resistance can be used instead.

**The Charging Circuit**

See Fig. 1, a basic R-C charging circuit. This circuit is generally well covered and "beat to death" in elementary electronics texts. When the switch S1 is closed and S2 is opened, voltage V is applied to the circuit. C1 has initially (and ideally) zero voltage across it and an initial current equaling V/R flows. However, the voltage across C1

starts to rise, and now the voltage across R1 is slightly less. This causes the charging current to drop. This process continues, the current dropping as the capacitor charges toward a final value equal to the voltage V. The exact waveform of the current is given by the mathematical plot of the function  $e^{-\alpha t}$  where  $\alpha = 1/RC$  and  $t =$  time.

If one writes the loop equations for this circuit as follows:

$$V = IR + Q/C$$

where  $I = i(t)$  a function of time;  $Q =$  charge on capacitor; and the quantities  $V =$  supply volts,  $C =$  Capacitance,  $R =$  resistance are all constant, then:

$$V - I(t)R = Q/C$$

If V (supply voltage) is constant and

the value of C is also constant, then remembering that the current I is defined as the rate of flow of charge per unit time:

$$\Delta V/\Delta T - [dI(t)/\Delta T] R = (dQ/\Delta T) / C$$

Remember,  $\Delta$  symbolizes "change of." This can be expressed mathematically using derivatives. A derivative of a mathematical function is the rate of change of one variable (current) with respect to another variable (time). If the rate of change is rapid, the derivative is large. If the function is a constant (no change), the derivative is zero. If two functions are identical, then their derivatives at a point are equal. Therefore:

$$dV/dt - [di(t)/dt] R = (dQ/dt) / C$$

Now remember that current is the rate of flow of charge with respect to time past a given point. Therefore:

$$i(t) = dQ/dt$$

We said that the supply voltage V is constant and does not change with time so

$$dV/dt \text{ is zero}$$

Therefore:

$$- [di(t)/dt] R = i(t) / C$$

or dividing both sides by R

$$di(t)/dt = - i(t) / RC$$

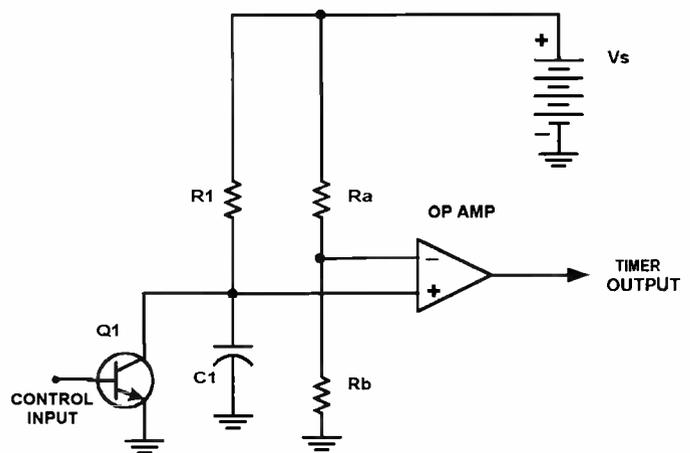


FIG 3 OP AMP TIMER



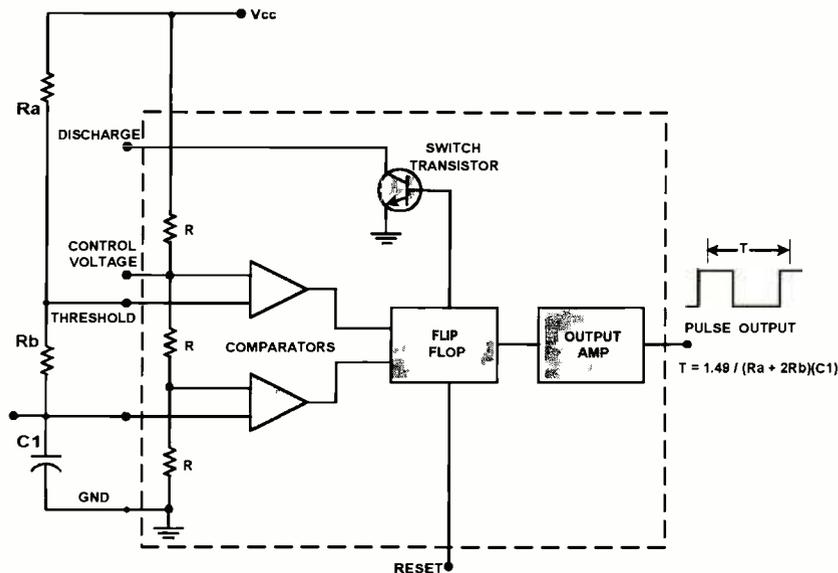


FIG 6 ASTABLE OPERATION OF NE555 TIMER

conducts, forward biasing the transistor Q1, turning it on. At about 9.8 volts, the zener diode and base of Q1 conduct heavily, taking the charging current from C1. C1 can charge no higher and ceases to draw current.

When power is turned off, the circuit is reset by C1 discharging through R1 into the now zero voltage supply. The time can be varied by changing R1 and C1, the zener voltage of D1, or the supply voltage. Note that the 2.2-K resistor and 100-µf capacitor have a time constant of 0.22 seconds. The actual delay time is about 0.37 seconds since the capacitor has to charge to about 82 percent of the supply voltage, which takes 1.7 time constants, and this is  $1.7 \times 0.22 = .374$  sec

If the 12-volt power supply malfunctioned and increased to 15 volts, the capacitor would have to charge to 9.8/15 or 64 percent of the supply voltage. This would take slightly more than 1 time constant, 1.015 to be exact; and this would decrease the delay time of this circuit to close to 0.22 seconds. Note the change in delay time with supply voltage. This change could cause premature turn on of the external controlled device with possible serious consequences. In practice, a critical function such as this would be handled by a microcontroller or other more sophisticated controller system, but the circuit shown demonstrates the principle.

### Op-Amps

Circuits using op-amps can also be used as timers. In these circuits, voltage

levels needed to set "trip points" can be derived from resistor-divider networks. The trip or reference voltages are determined by ratios of resistor values, rather than absolute voltage levels. This helps them to be independent of supply voltages. Now operating conditions are determined by percentages of power supply voltage, not fixed parameters. The reference voltages will directly track the power supply voltages, automatically compensating for variations.

A simple circuit is shown in Fig. 3. In this circuit an op-amp is used as a comparator. The reference voltage is derived from the power supply by the use of a resistive divider, Ra and Rb, and sets a level at the inverting input of the ampli-

fier. C1 normally would charge toward the power supply voltage Vcc, if not for the switching transistor Q1. For purposes of explanation, assume Ra = Rb. Then the reference level will be half the supply voltage. Initially the op-amp output voltage will be at its low limit, close to zero volts, since the capacitor voltage is held at zero by a switching transistor Q1 that is biased on.

When Q1 has its bias removed, it will cease conducting. Now C1 charges toward the supply voltage. When it reaches half of this voltage, its voltage will equal the voltage at the inverting input of the op-amp as set by Ra and Rb. When this voltage is passed, the op-amp, having very high gain, will switch; and its output will rise to nearly the supply voltage at this point. The time that this occurs will be at a time interval equaling 0.692 times the RC time constant, since at this point the voltage on the capacitor will reach half the supply voltage. The op-amp output voltage could be used to switch on Q1 by controlling the bias on it. This would either end the cycle or cause it to repeat; depending on the exact way it was done. A circuit called a flip-flop could be used to do this. A flip-flop is an elementary memory circuit having two stable states, much like a toggle switch, and is controlled by applying a level or pulse to its inputs. This principle is used in a very popular integrated circuit used as a timer, the NE555.

### The NE555 Timer

The NE555 timer and its various

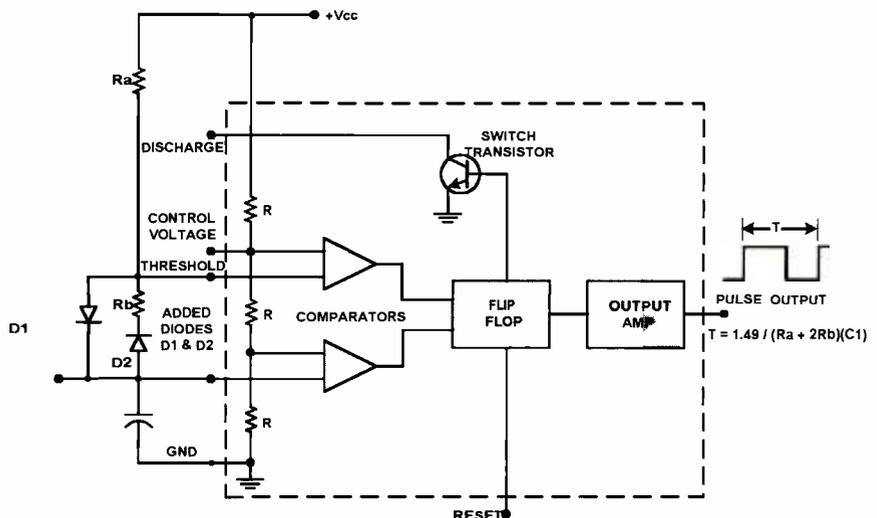


FIG 7 ASTABLE OPERATION OF NE555 TIMER WITH DUTY CYCLE CONTROL

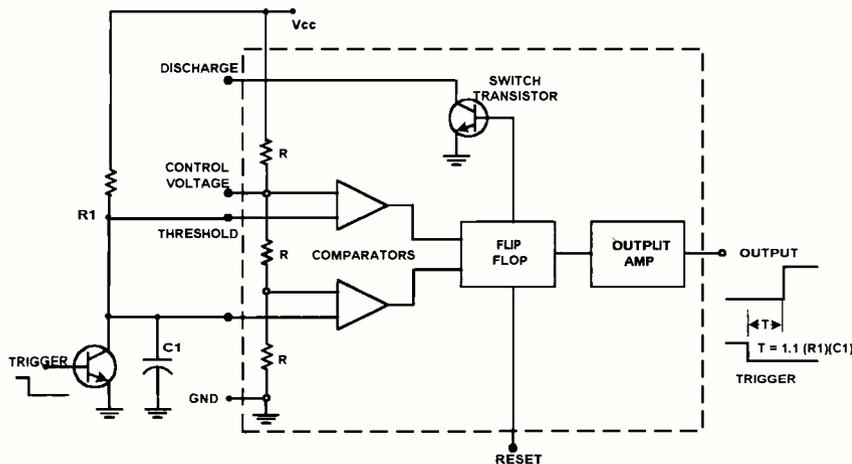


FIG 8 TIME DELAY OPERATION OF NE555 TIMER

related types are probably among the ten most popular and widely used IC devices of all time. The NE555 has existed for about thirty years and is a staple among experimenters. While the 555 is available in bipolar and CMOS types (7555), the CMOS versions may prove to be somewhat more useful for many experimenter applications. This is because the higher circuit impedances allow more reasonable values of R and C components, especially important where long time delays are required. These devices come in a DIP (dual inline) 8-pin package in thru-hole and surface-mount.

A dual timer, the NE556, is also available, as well as a quad version, the NE558. The NE555 is very versatile and can be used as an astable (free running) timer/oscillator or as a one-shot (monostable) triggered timer. Figure 4 is a block diagram of the 555 device. It consists of two comparator amplifiers, a flip-flop, an output driver and a discharge transistor. A single external resistor, R, and capacitor, C, determine the

time interval. The comparators are internally referenced by an internal resistive voltage divider at  $\frac{1}{3}$  and  $\frac{2}{3}$  of the supply voltage. The  $\frac{2}{3}$  voltage is brought out to a separate pin. This pin is often unconnected or bypassed to ground in many applications. The collector of the discharge transistor is also brought out to a separate pin. A reset input is provided to reset the flip-flop. The bipolar NE555 can output 200 mA with a 15-volt supply, enough to directly drive many small loads. The pulse width can be from about a half a microsecond up to around an hour, depending on external components. About 20 to 30 minutes is about the maximum practical limit. Beyond this limit, an external count-down scheme using a frequency divider can be implemented.

### Generating A Pulse

A circuit to generate a pulse is shown in Fig. 5. In this circuit, the flip-flop internal to the 555 is normally set so that the discharge transistor is conducting. A

negative going trigger or pulse is applied to the trigger input. This input is that of the lower comparator and is biased at  $\frac{1}{3} V_{cc}$ . The trigger must be negative going so as to drive the input below  $\frac{1}{3} V_{cc}$ . Generally an AC-coupling capacitor is used so as not to upset the DC level here. This causes the comparator to change the state of the flip-flop, cutting off the discharge transistor. External capacitor C1 starts to charge through R1 until it reaches  $\frac{2}{3} V_{cc}$ . This takes about 1.1 time constants. At this point, the upper comparator changes its state and resets the flip-flop. This causes the internal discharge switch transistor to turn on, discharging C1. Note that the trigger to the lower comparator must be removed by this time, or else erroneous operation will result. Since the discharge transistor is directly connected to the threshold input and across the capacitor, this action is very rapid.

The generated pulse appears at the device-output pin and has a period of close to 1.1 RC. This circuit can be used to trigger another timer circuit. Triggering in this mode occurs on the negative-going edge of the trigger pulse. Once the circuit is triggered, it will complete its cycle with no regard to extra triggers during this period. Resetting can be done via a pulse applied to the reset input. This resets the flip-flop and turns on the discharge transistor.

The 555 can be used as an oscillator, with one extra resistor needed to do this. Figure 6 shows this configuration. The trigger pin is tied to the threshold pin. R1 is split into two parts, Ra, and Rb, and the discharge transistor is connected to their junction. When power is applied, the capacitor, C1, charges toward  $V_{cc}$  until  $\frac{1}{3} V_{cc}$  is reached. At that point, the discharge transistor turns on, discharging C1 through Rb until  $\frac{1}{3} V_{cc}$  is reached. Then, the comparator trips; and the discharge transistor turns off. Now the capacitor, C1, charges again to  $\frac{2}{3} V_{cc}$  until this voltage is reached. The capacitor voltage will switch between  $\frac{1}{3} V_{cc}$  and  $\frac{2}{3} V_{cc}$ . Note that on startup the first cycle is longer, since the capacitor must charge between zero and  $\frac{2}{3} V_{cc}$ . On subsequent cycles, it starts from  $\frac{1}{3} V_{cc}$ , so the time for charging will be shorter. The formula for the frequency is given by:

$$F = 1.49 / (Ra + 2 Rb)C1$$

Note that by varying the ratio of Ra  
(Continued on page 56)

## NORTH COUNTRY RADIO: A HAVEN FOR WIRELESS BUFFS

Graf and Sheets are no strangers to the pages of Gernsback. Their educational projects, such as the *RF-Field Strength Meter* and the *MPX2000 FM Transmitter*, can be found at **North Country Radio**. Established in 1986, this company offers projects related to amateur TV transmitters/receivers, AM and FM transmitters/receivers, video cameras, and numerous other subjects. Visit the Web site at [www.northcountryradio.com](http://www.northcountryradio.com) for more information.

**Ordering Information:** PO Box 53, Wykagyl Station, New Rochelle, NY 10804-0053; Voice: 914-235-6611; Fax: 914-576-6051; e-mail: [Rgraf30832@aol.com](mailto:Rgraf30832@aol.com).

**Engineering and Technical Support**  
PO Box 200, Hartford, NY 12838  
Voice/Fax: 518-854-9280  
e-mail: [support@northcountryradio.com](mailto:support@northcountryradio.com)

## A Clue, Mr. Inductor

Well, with the inductor removed or open, the diode charges the capacitor as it would in a power supply and results in the diode output being clamped to zero volts. It actually makes sense. First, I try winding an inductor, but even with as many turns of #32 wire as I can fit on a ½-watt resistor body, the value must be way too low as the output is still dead.

Rummaging around in my inductor drawer, I locate one that looks kind of similar. Unmarked, but of approximately the right size and construction (I really don't have a great stock of inductors). The original is marked 471, which I assume to be 470  $\mu$ H; but I didn't photocopy the page of the *Sams' Photofact* with inductor ratings, unfortunately. The results with my unmarked replacement are mixed—the picture is there (well, that really doesn't prove anything), but it seems a little bright. This signal looks fine; maybe the bright picture is my imagination. OK, try a different larger one. This even measures the same on my ohmmeter as the original should (like that means anything).

However, the picture now appears normal. Since the poor lonely inductor sitting on my bench still measures infinity ohms, I am confident that this is indeed the problem. Exactly what mechanism results in a delayed start inductor is not quite clear. It is not heat, as there is no time for any thermal effects and the power dissipation in the inductor is about as close to zero as one can imagine. Is it simply the voltage pulses appearing across some kind of marginal semiconductor-like junction formed by corrosion between the coil wire and the leads that eventually results in good contact?

Attempting to 'disassemble' the broken inductor simply results in broken inductor pieces everywhere so I will never really know for sure what happened, until another one of the half dozen or so similar inductors in the TV decides to do its open circuit thing.

Maybe some day I will actually order the correct replacements for both of the dud inductors—this new unmarked one and the homemade inductor that fixed the previous messed up color problem. For now, it seems to be fine and the TV shows won't be any better with the proper replacement parts anyhow.

## Reflections

Comments—No doubt next time (sure, if there is a next time), I will test

all the similar inductors first! What could possibly lead to a batch of unreliable inductors is another one of those mysteries of the universe. After all, an inductor is just a coil of wire soldered to a couple of leads. There is no thermal or mechanical shock, and the circuit is very low power in any case. The TV is not in a damp location or subject to any other kind of abuse that I know of, though based on the appearance of the innards of the inductor, some type of deterioration may have taken place.

How should one diagnose a problem of this type? In hindsight, I guess testing components in the vicinity of the Lum/Chroma Proc after waiting a week and with power off would make sense. But, some of the elapsed time was required to localize the problem to that chip. However, once it was clear that one of the signals to U700 was messed up, the ohmmeter checks would have greatly reduced the additional required debug time. Would freeze spray have worked? Perhaps—if anyone had thought to hit the inductor. There were no electrolytic capacitors anywhere in the circuitry around U700.

## Wrapup

Some might consider this set an antique as it was new around 1980. As of 2002, the set continues to function without any more inductors dying. I'm sure many readers would consider a 22-year-old TV something that belongs in a museum. However, while it doesn't have some of the features of a modern TV (heck, it doesn't even have a remote control as I wasn't willing to pay the extra \$50 for that—not being standard in 1980!), the picture and sound quality is still quite good.

I welcome feedback of almost any kind (via e-mail only please to sam@repairfaq.org). And there is much more repair, general electronics, and laser and optics information on my Web site, [www.repairfaq.org](http://www.repairfaq.org). 

## ALL ABOUT

(continued from page 40)

to Rb, the duty cycle can be varied. However, there is a problem. Since the charging path is through Ra + Rb and the discharge path through Rb, they can never be equal. This makes a 50 percent duty cycle unachievable with this circuit, since Ra + 2 Rb always will be > Ra unless Ra is made to be zero. This problem can be corrected by using two diodes (1N914 types, etc.) to steer the charge and discharge paths through only Ra and Rb, respectively. In practice, this allows less than 5% to more than a 95 % duty cycle to be achieved. Note that due to device limitations Rb must be greater than about 3k $\Omega$  for reliable performance. This is shown in Fig. 7. Ra and Rb could be incorporated into a potentiometer to adjust the duty cycle, with C being used to set the frequency.

## Time Delays

Another mode of operation is that of providing a time delay. In monostable operation, a pulse lasting for a predetermined time is generated immediately on triggering. The output goes high immediately and times out after the predetermined time. In time-delay operation, it is desired to have a state change only after a delay. In this mode (see Fig. 8), the internal discharge transistor is not used. The threshold and trigger are tied together. The capacitor C is instead discharged upon the application of a triggering pulse to the transistor. When this transistor is turned on, C is kept discharged. This keeps the trigger and threshold low, and the timer output is forced low. When a negative-going level is placed on the base of the triggering transistor, it is cut off. The capacitor charges toward the supply voltage; and then when the threshold voltage is reached, the output now changes state. The output will then remain unchanged until the triggering transistor is turned on.

Circuits using this device will be discussed in the next part of this article. 

## Get your copy of the CRYSTAL SET HANDBOOK



Go back to antiquity and build the radios that your grandfather built. Build the "Quaker Oats" type rig, wind coils that work and make it look like the 1920's! Only \$10.95 plus \$4.00 for shipping and handling. Clagg Inc., PO Box 12162, Hauppauge, NY 11788. USA Funds ONLY! USA and Canada—no foreign orders. Allow 6-8 weeks for delivery. MA01

# BE A TEACHER. BE A HERO.

Call  
1-800-45-TEACH.