

# An Efficient Procedure for Narrowband Bandpass Filter Design

Here is a review of lowpass-to-bandpass transformations with an example filter operating at 5 GHz


By **Zlatoljub D. Milosavljevic** and **Miodrag V. Gmitrovic**  
 Faculty of Electronic Engineering, University of Nis, Yugoslavia

**B**andpass filters (BPF) may be constructed by cascading lowpass (LP) and highpass (HP) filters. This type of realization is suitable for devices with wide bandwidths but is not convenient for the realization of narrowband BPFs, that is, for bandwidths of less than about 10 percent [1]. This is related to the high degree (number of poles and zeros) needed for the filters to achieve good selectivity. The cascaded type of realization causes large insertion losses and poor amplitude flatness.


Cauer and generalized Chebyshev [2, 3] LP prototype filters are very good starting points for the design of selective BPFs. This article discusses the BPF network transformations suitable for physical realization [4, 5]. These transformations are based on the insertion of redundancy ideal transformers in BPFs and the use of Norton's equivalent networks [6].

A proper choice of transformer transformation ratio produces a network with a minimum spread of element values. A new and efficient numerically-based procedure for getting an exact solution of optimal parameter  $t$  in closed form is presented in [5]. The lumped element network ultimately obtained has no transformers and is very convenient for the design of microwave filters, duplexers and multiplexers using printed circuit technology.

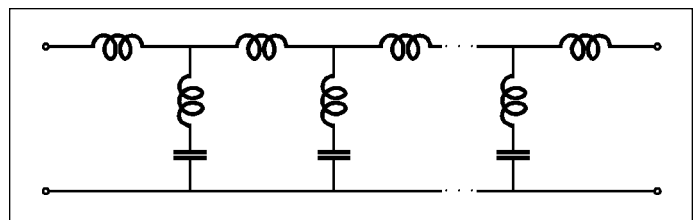This article also discusses the efficient transformation for the design of a narrowband bandpass filter with transmission lines. The use of suspended substrate techniques [1, 7] allows us to use highly selective prototypes, which can achieve excellent performances. The suspended



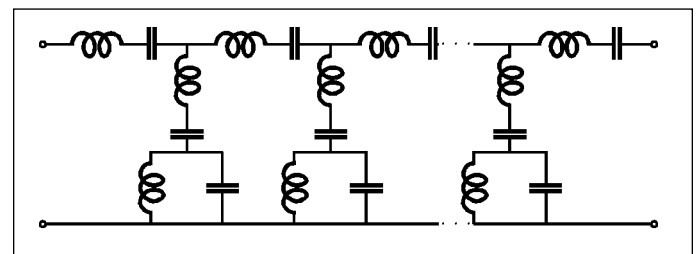▲ Figure 1. LP prototype filter with real transmission zeros.




▲ Figure 2. BPF structure.

substrate stripline (SSS) narrowband BPF design procedure is introduced by an example filter with excellent characteristics.
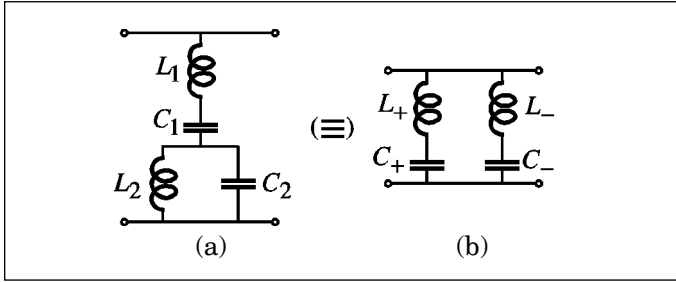
## Lumped element network development

A typical LP prototype filter with real transmission zeros is shown in Figure 1. The BPF in Figure 2 is obtained from the use of a well-known frequency transformation on element immittances of the LP prototype filter.

The transformed network in Figure 2 has a large spread of element values and shunt structures unsuitable for practical construction. Since these are very difficult to realize directly, a more convenient equivalent circuit must be found. Such an equivalent structure has been derived [1] and is shown in Figure 3b.



▲ Figure 3. Alternative shunt element configurations.

The element values  $L_+$ ,  $C_+$ ,  $L_-$ ,  $C_-$  of the network in Figure 3b, are defined by relations [1]

$$\alpha = L_1 C_1 + L_2 C_2 + L_2 C_1$$

$$b = L_1 L_2 C_1 C_2$$

$$\alpha_+ = \sqrt{\frac{\alpha}{2} + \left(\frac{\alpha}{2}\right)^2} - b$$

$$\alpha_- = \frac{\alpha}{2} + \sqrt{\left(\frac{\alpha}{2}\right)^2 - b}$$

$$\beta_+ = \frac{C_1 L_2 C_2 - C_1 \alpha_+}{\alpha_- - \alpha_+}$$


$$\beta_- = \frac{C_1 L_2 C_2 - C_1 \alpha_-}{\alpha_+ - \alpha_-}$$

$$C_+ = \beta_+, C_- = \beta_-,$$


$$L_+ = \frac{\alpha_+}{\beta_+} \text{ and } L_- = \frac{\alpha_-}{\beta_-}$$

By transforming the network in Figure 2 into that of Figure 3, a more realizable network can be obtained. The spread of element values is smaller than in the original BPF, but it is still quite large. The simplest third degree network obtained in this manner is shown in Figure 4. This structure has the additional disadvantage that branches connected in parallel cause unwanted parasitic capacitance and inductance [6].

The parasitic effects can be removed and the spread of element values decreased by insertion of redundant ideal transformers with the transformation ratio  $t$ . For the network in Figure 4, two ideal transformers can be inserted as in Figure 5. As we can see, both networks have the same transfer function. Ideal transformers can be eliminated by Norton's equivalent networks [6] given in Figure 6. Equivalencies should be used twice on the parts of the network in Figure 5 designated with large brackets. It should be noted that one of the serial impedances in Norton's equivalent network always has a negative value. In many instances it is possible, using the other part of the network, for the ultimately transformed network to have all positive element values. The network in Figure 7 is obtained by transforming the net-

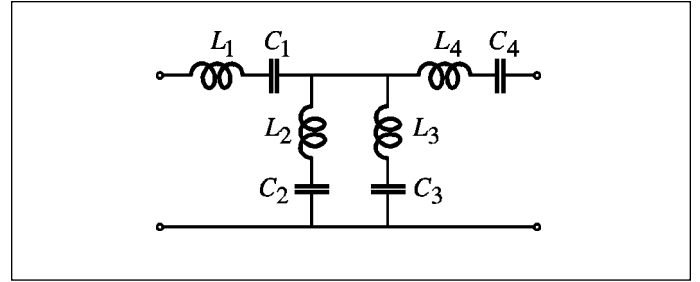

▲ Figure 4. Transformed BPF.

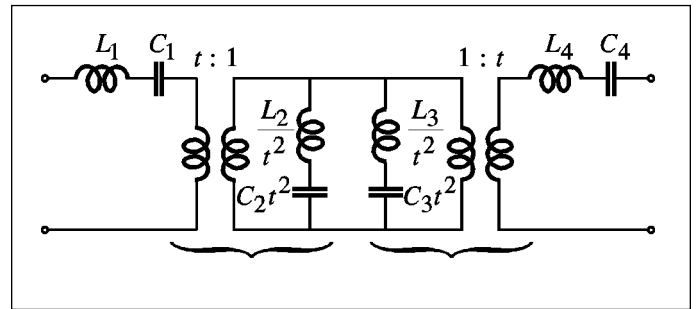

(1) ▲ Figure 5. BPF with ideal transformers.

work in Figure 5 with equivalencies in Figure 6. The last BPF element values are

$$\begin{aligned} L'_1 &= L_1 + L_2 \frac{t-1}{t}, \frac{1}{C'_1} = \frac{1}{C_1} + \frac{t-1}{C_2 t} \\ L'_2 &= \frac{L_2}{t}, C'_2 = C_2 t \\ L'_3 &= (L_2 + L_3) \frac{1-t}{t^2}, \frac{1}{C'_3} = \left(\frac{1}{C_2} + \frac{1}{C_3}\right) \frac{1-t}{t^2} \\ L'_4 &= \frac{L_3}{t}, C'_4 = C_3 t \\ L'_5 &= L_4 + L_3 \frac{t-1}{t}, \frac{1}{C'_5} = \frac{1}{C_4} + \frac{t-1}{C_3 t} \end{aligned} \quad (2)$$

A sufficient condition for all the network element values in Figure 7 to be positive is

$$\max \left\{ \frac{L_2}{L_1 + L_2}, \frac{C_1}{C_1 + C_2}, \frac{L_3}{L_3 + L_4}, \frac{C_4}{C_3 + C_4} \right\} < t < 1 \quad (3)$$

By inserting the two ideal transformers in the network shown in Figure 5, the resulting network has two additional elements. Element values depend on the value of the redundancy factor  $t$ , and the last network is without transformers. By inserting two transformers with different transformation ratios  $t_1$  and  $t_2$ , it may be possible for the transformed network to have only one additional element. In this case the transformed net-

work is also without transformers, but has different loads,  $R_S \neq R_L$ .

The optimum value of parameter  $t$  can be found in closed form [5]. The first step in getting optimal  $t$  is calculating maximum and minimum values of inductances and capacitances for the discrete values of the parameter  $t$  from the range defined by Equation (3). If the aim of the BPF design is to minimize the ratio between the maximum and minimum values of reactive elements, it can be noted that for the chosen step  $\Delta t$ , there is a value  $t$  for which this condition is fulfilled. The next step is equating minimum or maximum values of inductances or capacitances that change values in the vicinity of the chosen value  $t$ . This gives an equation which yields the optimum value of  $t$ .

### Distributed element network development

The next step in designing a narrowband BPF is to transform the lumped element BPF into one with distributed elements. Inductors are replaced with short-circuited capacitors and capacitors with open-circuited transmission lines. In the case of the third degree BPF given in Figure 7, a transformed BPF with ideal transmission lines is given in Figure 8. The electrical length of all transmission lines is  $\theta_c = 45^\circ$  at the band center frequency  $f_c$ .

The BPF obtained this way usually has transmission lines with characteristic impedance values that are too high to be practical for realization in printed circuit technology. Therefore, a transformation should be applied on the last BPF. The impedance values of the filter could be scaled to the lower values:


$$Z'_{ci} = \frac{Z_{ci}}{n}, i = 1, 2, \dots, 10 \quad (4)$$

and gyrators should be introduced at input and output to transform all impedances to the characteristic impedance at the input and output port,  $Z_c$ . The gyrators' constant is:


$$r = \frac{Z_c}{\sqrt{n}} \quad (5)$$

Parameter  $n$  from the equations (4) and (5) is a positive number.

A ladder BPF network can be efficiently characterized by ABCD parameters, as seen in Figure 9. For reciprocal networks  $AD - BC = 1$ , and for symmetrical networks  $A = D$ . The use of ABCD parameters at microwave frequencies is not very convenient from the measurement point of view. Scattering matrix formulation is a more general method of representing microwave networks. Therefore, conversion from the ABCD-matrix to the S-matrix for reciprocal and symmetrical network from Figure 9, gives [8]:

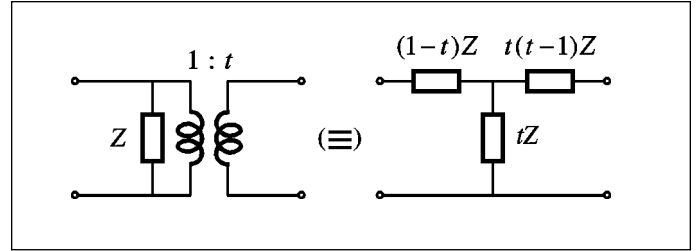

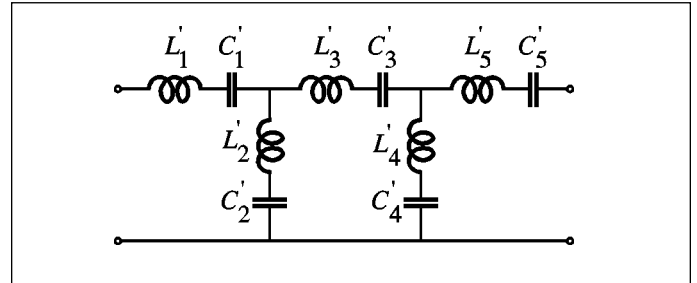▲ Figure 6. Norton's equivalent networks.




▲ Figure 7. BPF structure ultimately obtained.


$$S_{11} = S_{22} = \frac{B - CZ_c^2}{2AZ_c + B + CZ_c^2} \quad (6)$$

$$S_{12} = S_{21} = \frac{2Z_c}{2AZ_c + B + CZ_c^2} \quad (7)$$

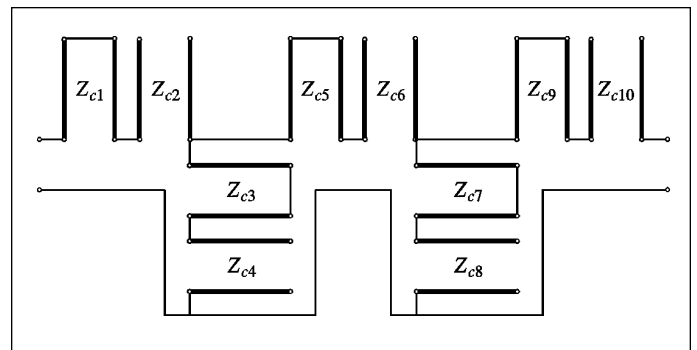A transformed network from Figure 9 with scaled impedance values as in (4). This network with two gyrators defined by (5) is shown in Figure 10. It can be shown that this network has the next S-matrix



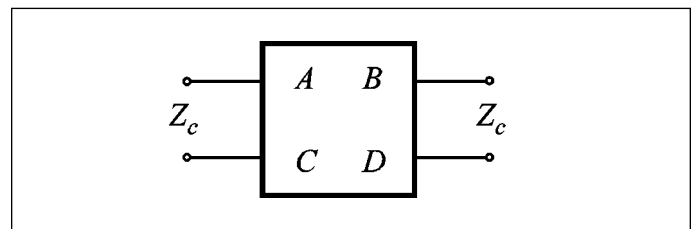▲ Figure 8. The BPF with ideal transmission lines.



▲ Figure 9. A generalized two-port network.

$$S_{11}^g = S_{22}^g = -S_{11} = -S_{22} \quad (8)$$

$$S_{12}^g = S_{21}^g = S_{12} = S_{21} \quad (9)$$

Equations (8) and (9) show that the transformed network has the same  $S$ -parameters as the original network. The only difference is a phase shift of  $180^\circ$  for the reflection coefficients  $S_{11}^g$  and  $S_{22}^g$ . This fact enables the use of this network for the BPF realization. In the case of a narrowband BPF it is possible to realize gyrators as low impedance transmission lines one-quarter wavelength long at band center, with characteristic impedance  $Z'_c = r$  and electrical length  $\theta = 90^\circ$  at the center frequency  $f_c$ .

In the next step, series connected, short-circuited and open-circuited transmission lines in parallel branches should be replaced with cascade-connected transmission lines to obtain shunt stubs suitable for practical realization. This is illustrated in Figure 11 and characteristic impedance values are defined by

$$Z_{c3} = Z_{c1} + Z_{c2}, Z_{c4} = \frac{Z_{c1}}{Z_{c2}} Z_{c3} \quad (10)$$

Another problem for printed circuit realization of the BPF is existence of short-circuited transmission lines in series branches. In the case of the third degree filter, those are scaled values  $Z'_{c1}$ ,  $Z'_{c5}$  and  $Z'_{c9}$ . This disadvantage can be removed by realizing these lines using short transmission lines with high characteristic impedance values  $Z_{ch}$  and electrical lengths:


$$\theta_i = \frac{Z'_{ci}}{Z_{ch}} \frac{180}{\pi} [^\circ], i = 1, 5, 9 \quad (11)$$

The final BPF structure with ideal transmission lines is given in Figure 12.

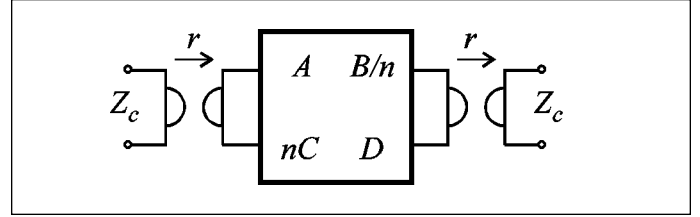
## BPF design example

A design procedure for BPF in SSS technology can be given by example. A narrowband BPF, with passband frequencies of  $f_1 = 4875$  MHz and  $f_2 = 5125$  MHz, is a particularly good design example. In this case, the center frequency is  $f_c = (f_1 f_2)^{1/2} = 4998.4373$  MHz and the bandwidth is approximately 5 percent of  $f_c$ . Cauey's LP prototype third degree filter given in Figure 13 is transformed into a bandpass prototype filter (BPPF) with the normalized center frequency  $\Omega_{cn} = 1$ . The LP prototype filter C0325-28 [9] has maximum attenuation in the pass-band  $\alpha_p = -0.2803$  dB, minimum attenuation in the stop-band  $\alpha_s = -30.4$  dB, and element values are  $L_{1p} = 1.221240$ ,  $C_{2p} = 0.985344$  and  $L_{2p} = 0.172857$ . From the Richards frequency transformation

$$\Omega_{cn} = \tan \theta_c = \tan \omega_c T \quad (12)$$



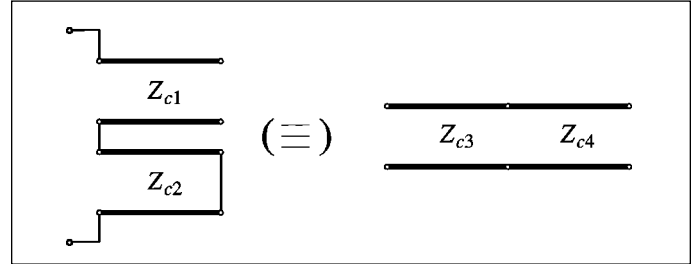▲ Figure 10. A transformed two-port network.



▲ Figure 11. Equivalent circuits.

the time delay  $T = 1/(8f_c) = 2.5008 \times 10^{-11}$  s can be calculated. The normalized bandwidth of the BPPF is  $B_n = \tan \omega_2 T - \tan \omega_1 T = 0.0786449$ . Applying the previously presented procedure, the LP prototype filter given in Figure 13 can be transformed into a BPPF as shown in Figure 7.

The optimum value of parameter  $t$  can be found in closed form [5]. Equation (3) gives  $0.2382307 < t < 1$ . The first step in getting an optimum value of  $t$  is calculating maximum and minimum values of inductances and capacitances for the discrete values of the parameter  $t$ . It is shown in Table 1.

If the aim of the BPF design is to minimize the ratio between the maximum and minimum values of reactive elements, it can be seen from Table 1 that for  $0.3 \leq t \leq 0.9$  and step  $\Delta t = 0.1$ ,  $t = 0.6$ . Maximum and minimum values of reactive elements change the values in the vicinity of  $t = 0.6$ . Therefore, it is necessary to calculate extreme values for  $t = 0.55$  and  $t = 0.65$ .

For  $t = 0.55$ , the values are

$$\begin{aligned} L_{\max} &= L'_3 = 13.1974, L_{\min} = L'_2 = 7.3001, \\ C_{\max} &= C'_4 = 0.136984, C_{\min} = C'_3 = 0.0757725, \\ L_{\max}/L_{\min} &= C_{\max}/C_{\min} = 1.808 \end{aligned}$$


For  $t = 0.65$ , the values are

$$\begin{aligned} L_{\max} &= L'_1 = 13.3666, L_{\min} = L'_2 = 6.17701, \\ C_{\max} &= C'_4 = 0.161891, C_{\min} = C'_5 = 0.0748134, \\ L_{\max}/L_{\min} &= C_{\max}/C_{\min} = 2.164 \end{aligned}$$

To obtain a closed form for the exact values of optimal parameter  $t$ , it is necessary to notice that for  $t < 0.55$  the maximum inductance value is  $L_{\max} = L'_3$ , and for  $t > 0.55$  it is  $L_{\max} = L'_1$ . Equating  $L'_3 = L'_1$ , the optimal

$t$	$L_{\max}$	$L_{\min}$	$L_{\max}/L_{\min}$	$C_{\max}$	$C_{\min}$	$C_{\max}/C_{\min}$
0.3	$L'_3 = 69.0012$	$L'_5 = 4.19663$	16.442	$C'_1 = 0.238287$	$C'_3 = 0.0144925$	16.442
0.4	$L'_3 = 33.2684$	$L'_5 = 8.24374$	4.035	$C'_1 = 0.121304$	$C'_3 = 0.0300585$	4.035
0.5	$L'_3 = 17.7432$	$L'_2 = 8.03011$	2.209	$C'_4 = 0.124531$	$C'_3 = 0.0563597$	2.209
0.6	$L'_1 = 12.8518$	$L'_2 = 6.69176$	1.920	$C'_4 = 0.149438$	$C'_5 = 0.0778099$	1.920
0.7	$L'_1 = 13.8078$	$L'_3 = 5.43158$	2.542	$C'_3 = 0.184108$	$C'_5 = 0.0724229$	2.542
0.8	$L'_1 = 14.5248$	$L'_3 = 2.77237$	5.239	$C_3 = 0.360702$	$C'_5 = 0.0688479$	5.239
0.9	$L'_1 = 15.0824$	$L'_3 = 1.09526$	13.771	$C'_3 = 0.913027$	$C'_5 = 0.0663024$	13.771

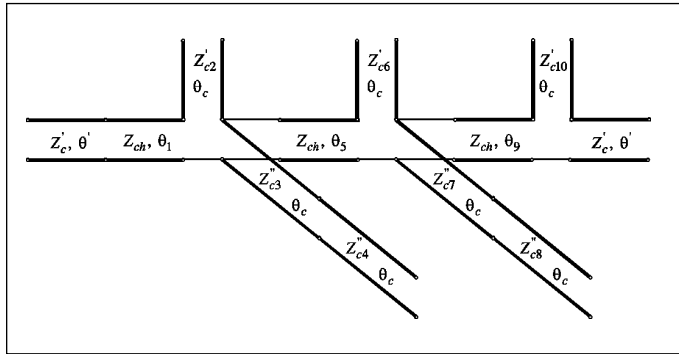▲ **Table 1.** The extreme element values for  $0.3 \leq t \leq 0.9$ .



▲ **Figure 12.** The approximated BPF structure with ideal transmission lines.


redundancy parameter

$$t = -\frac{L_3}{2(L_1 + L_2)} + \sqrt{\left[\frac{L_3}{2(L_1 + L_2)}\right]^2 + \frac{L_2 + L_3}{L_1 + L_2}} \quad (13)$$

is obtained and the calculated value is  $t = 0.560862$ . The same value could be calculated from the requirement  $C'_5 = C'_3$ , because we started from the symmetrical LP prototype filter. The element values for the BPPF are  $L'_1 = 12.3849$ ,  $C'_1 = 0.0852805$ ,  $L'_2 = 7.15873$ ,  $C'_2 = 0.115486$ ,  $L'_3 = 12.3849$ ,  $C'_3 = 0.0807437$ ,  $L'_4 = 8.65905$ , and  $C'_5 = 0.0807437$ . The ratio between the maximum and minimum values is  $L_{\max}/L_{\min} = C_{\max}/C_{\min} = 1.73$ . The obtained structure of the BPPF is very convenient for realization in the printed circuit technology, because it has a minimum spread of element values.

The next step in SSS BPF designing is transforming the BPPF into the BPF with ideal transmission lines. The characteristic impedance at the input and output port is  $Z_c = 50 \Omega$ . This BPF is shown in Figure 8. All transmission lines have the same electrical lengths of  $\theta_c = 45^\circ$  at the center frequency  $f_c$ . The characteristic impedance values are
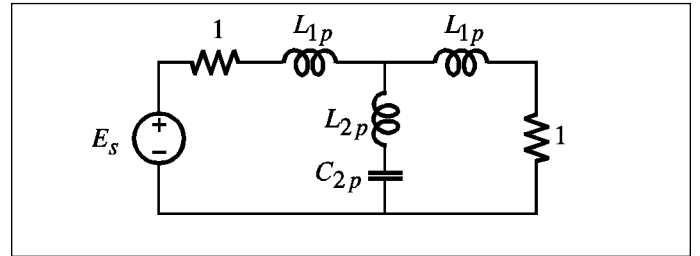
$$\begin{aligned} Z_{c1} &= L'_1 Z_c = 619.245 \Omega, Z_{c2} = Z_c / C'_1 = 586.3005 \Omega, \\ Z_{c3} &= L'_2 Z_c = 357.9365 \Omega, Z_{c4} = Z_c / C'_2 = 432.9525 \Omega, \\ Z_{c5} &= L'_3 Z_c = 619.245 \Omega, Z_{c6} = Z_c / C'_3 = 619.24336 \Omega, \end{aligned}$$



▲ **Figure 13.** Double terminated LP prototype filter.

$$\begin{aligned} Z_{c7} &= L'_4 Z_c = 432.9525 \Omega, Z_{c8} = 357.9543 \Omega, \\ Z_{c9} &= L'_5 Z_c = 586.3 \Omega, \text{ and} \\ Z_{c10} &= Z_c / C'_5 = 619.24336 \Omega \end{aligned}$$

It can be seen that transmission lines have too high characteristic impedance values to be practical in SSS technology. Therefore, a transformation should be applied on the last BPF by scaling impedance values and introducing gyrators as described earlier. For this example,  $n = 16$  in equations (4) and (5), and the electrical length of the gyrators is  $\theta = 90^\circ$  at the center frequency  $f_c$ .

Shunt stubs suitable for practical realization are obtained by using the transformation given in Figure 11 and equation (10).

Short-circuited transmission lines in series branches may be realized using short transmission lines with high characteristic impedance,  $Z_{ch} = 150 \Omega$ , and electrical lengths given in Equation (11).

The final BPF structure with ideal transmission lines is shown in Figure 12. The element values are

$$\begin{aligned} Z'_c &= 12.5 \Omega, Z_{ch} = 150 \Omega, Z'_{c2} = 36.643781 \Omega, \\ Z'_{c3} &= 49.430588 \Omega, Z'_{c4} = 59.790262 \Omega, \\ Z'_{c6} &= 38.70271 \Omega, Z'_{c7} = 49.430495 \Omega, \\ Z'_{c8} &= 40.865742 \Omega, Z'_{c10} = 38.70271 \Omega, \\ \theta &= 90^\circ, \theta_1 = 14.783386^\circ, \theta_c = 45^\circ, \\ \theta_5 &= 14.783386^\circ, \theta_9 = 13.996881^\circ \end{aligned}$$

All electrical lengths are calculated at  $f = f_c$ .

The next step in the BPF design is the calculation of real printed circuit parameters with SSS and broadside coupled SSS (BCSSS) transmission lines. The chosen

	$Z'_c$ $\theta$	$Z_{ch}$ $\theta_1$	$Z'_{c2}$ $\theta_c$	$Z''_{c3}$ $\theta_c$	$Z''_{c4}$ $\theta_c$	$Z_{ch}$ $\theta_5$	$Z'_{c6}$ $\theta_c$	$Z''_{c7}$ $\theta_c$	$Z''_{c8}$ $\theta_c$	$Z_{ch}$ $\theta_9$	$Z'_{c10}$ $\theta_c$
$w$ (mm)	27.11	0.58	3.087	5.39	4.09	0.58	5.706	5.39	6.99	0.58	8.889
$l$ (mm)	14.51	2.15	4.542	6.97	6.91	2.15	3.355	6.97	7.01	2.03	2.361

▲ **Table 2. Physical dimensions of SSS and BCSSS transmission lines for BPF.**

substrate is Cu-Flon with relative dielectric constant  $\epsilon_r = 2.1$ , substrate thickness  $h = 0.7874$  mm, conductor thickness  $t = 0.0127$  and upper and lower ground plane to substrate spacing  $h_u = h_l = 1.7$  mm. All transmission lines except  $Z'_{c2}$ ,  $Z'_{c6}$ , and  $Z'_{c10}$  are synthesized by using SSS transmission lines in the LineCalc program. Open-circuited transmission lines with the characteristic impedances  $Z'_{c2}$ ,  $Z'_{c6}$ , and  $Z'_{c10}$  are modeled with BCSSS transmission lines [10] by use of the tuning and optimization procedure in the Libra program. The calculated width and length values of all transmission lines are given in the Table 2.

The last step is drawing the BPF layout in the GasStation program. Calculated transmission characteristics of the designed filter are shown in Figure 14. The given characteristics are for the filter in Figure 8 (BPFIT), for the filter in Figure 12 (BPFITA) and for the filter in suspended substrate technology (BPFSSS). It can be seen that the designed filter in SSS technology corresponds very well to the filters with ideal transmission lines. The layout for designed filter is shown in Figure 15. The designed filter should be realized and tested very soon and measured characteristics will be given in a future article.


## Conclusion

This article has presented A design technique for a physically realizable selective band-pass filter. This technique enables narrow-band SSS filters to be designed. In


this article, transformations of BPFs have been given based on the insertion of ideal transformers and the use of Norton's equivalencies. The closed form of the optimal redundancy parameter  $t$  has been obtained. A few very efficient transformations and approximations convenient for the design of BPF with transmission lines have been given. The design procedure has introduced by one example of BPF designed in SSS and BCSSS technology. It is shown that a BPF can be designed very efficiently by using the presented technique. ■

## References

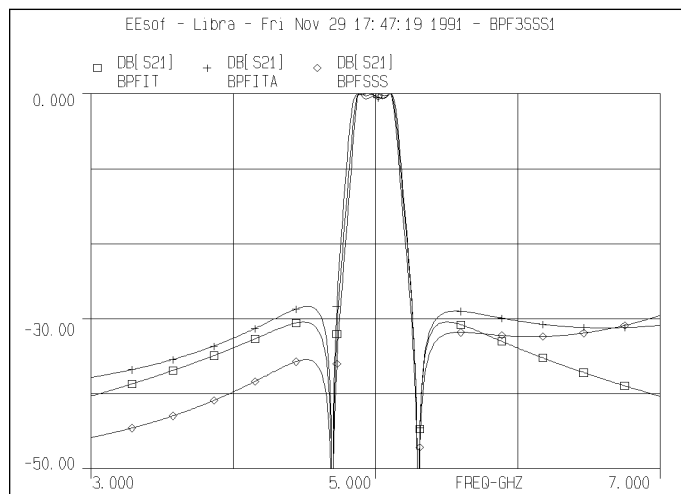1. C.I. Mobbs and J.D. Rhodes, "A Generalized Chebyshev Suspended Substrate Stripline Bandpass Filter," *IEEE Trans. on MTT*, Vol. MTT-31, No. 5, 1983.
2. Z.D. Milosavljevic, M.V. Gmitrovic and B.M. Djuric, "The Generalized Chebyshev Prototype Diplexer," *Proceed. of the 8th Int. Symp. ISTET*, Thessaloniki, Greece, 1995.
3. Z.D. Milosavljevic and M.V. Gmitrovic, "A Class of Generalized Chebyshev Low-Pass Prototype Filter Design," *AEÜ Int. J. Electron. Commun.*, Vol. 51, No. 6, 1997.
4. M.V. Gmitrovic and Z.D. Milosavljevic, "Band-Pass Filters with a Minimum Spread of Element Values," *Proceed. of the 10th Int. Symp. ISTET*, Magdeburg, Germany, 1999.
5. Z.D. Milosavljevic and M.V. Gmitrovic, "Designing Band-Pass Filters with Optimal Redundancy



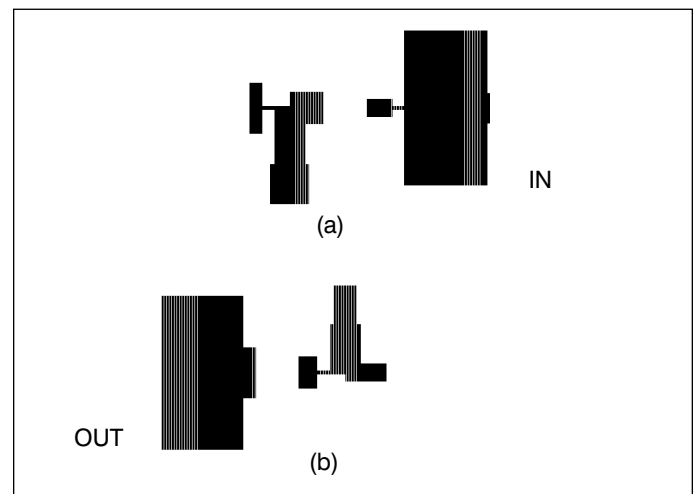▲ **Figure 14. Transmission characteristics of the designed filters.**



▲ **Figure 15. BPF layout a) upper side and b) lower side.**

Parameters," *Proceed. of the 4th Int. Conf. TELSIKS*, Nis, Yugoslavia, 1999.

6. D. S. Humpherys, *The Analysis, Design and Synthesis of Electrical Filters*, Prentice-Hall, Englewood Cliffs, NJ, 1970.

7. L. Jingshun, "Computer-Aided Design of Elliptic Function Suspended-Substrate Filters," *Proceed. of the Int. Conf. ICMMT*, Beijing, China, 1998.

8. K. C. Gupta, R. Garg and R. Chadha, *Computer-Aided Design of Microwave Circuits*, Artech House, Dedham, MA, 1981.

9. R. Saal and W. Entenmann, *Handbuch zum Filterentwurf*, Elitera, Berlin, 1979.

10. P. Bhartia and P. Pramanick, "Computer-Aided Design Models for Broadside-Coupled Striplines and Millimeter-Wave Suspended Substrate Microstrip Lines," *IEEE Trans. on MTT*, Vol. MTT-36, No. 11, 1988.

## Author information

Zlatoljub D. Milosavljevic studied electronic engineering at Nis University, and received his Dipl.-Ing. degree in 1993. In October



1993, he joined the Nis University Faculty of Electronic Engineering, Department of Telecommunications, where he is a teaching and research assistant. He received his M.Sc. degree in 1997 and is currently working towards the Ph.D. degree.

His main research interests are network synthesis, signal processing, filters, diplexers and multiplexers with lumped and distributed elements. He can be reached at the Faculty of Electronic Engineering, Beogradska 14, 18000 Nis, Serbia, Yugoslavia, Fax: +381 18 46 180, or by e-mail at: zlatko@elfak.ni.ac.yu.

Miodrag V. Gmitrovic received his Dipl.-Ing. and Ph.D. degrees in elec-

tronic engineering, from the University of Nis in 1967 and 1982 respectively. From 1967 to 1973, he was a research engineer at the Electronic Industries (Ei) Research



Institute. Since 1973 he has held a teaching position at the Nis University Faculty of Electronic Engineering, Department of Telecommunications, where he is Full Professor and Faculty Vice-Dean. His research interests include circuit theory, network synthesis, distributed network and filters. He can be reached by e-mail at: gmitrovic@elfak.ni.ac.yu.