

# Hybrid Frequency Synthesizer Combines Octave Tuning Range and Millihertz Steps

DDS and PLL techniques are combined in this high-resolution synthesizer


By Benjamin Sam

Analog Devices Northwest Laboratories

**M**icrowave synthesizers with wide tuning ranges and fine tuning steps are found in applications including RF signal generators, spectrum analyzers, communication transceivers, surveillance receivers and TV/CATV monitoring and test equipment. The advance of semiconductor technology has simplified the design of these microwave frequency synthesizers while reducing the cost, size and complexity. This article describes a simple implementation of such a synthesizer which delivers good phase noise and spurious performance along with an octave tuning range and fine tuning steps.

## Hybrid phase-locked loop overview

Figure 1 shows the block diagram of a microwave synthesizer consisting of a phase-locked loop with an octave-tuning voltage-controlled oscillator (VCO), a single-sideband (SSB) mixer and a direct-digital synthesizer (DDS). Support circuitries include a coarse-tuning digital-to-analog converter (DAC), a loop filter and a quadrature phase-splitter. Using the SSB mixer, the VCO output frequency is offset by that of the DDS before it is fed to the frequency divider of the PLL. By comparing the phase of the frequency-divided mixer output with that of a crystal-based reference and feeding back the error to correct the VCO frequency, the PLL

 

▲ Figure 1. Frequency synthesizer block diagram.

sets the coarse frequency steps via its divider value. The DDS controls the fine tuning of the VCO. An external crystal oscillator provides the reference frequency used by both the PLL and the DDS. Detailed operation of the PLL can be found in several texts [1-4].

## Frequency planning

The synthesizer presented here is intended to be used in both a 2.4 GHz RF signal generator and a 1 GHz spectrum analyzer. The VCO, and hence the synthesizer, will be tuned over the range of 1.2 - 2.4 GHz. The DDS generates a signal from 0.2 - 0.4 MHz, which is lowpass filtered to produce the offset frequency in millihertz steps. This offset frequency then goes through a quadrature phase-splitter to modulate a sample of the VCO output using the quadrature modulator. The resultant signal is then fed to the PLL



# FREQUENCY SYNTHESIZERS

*Direct-digital synthesizer (DDS)* — The DDS chip used in this project is the AD9832 from Analog Devices [6], running at a clock frequency of 25 MHz with 32-bit frequency resolution. The output frequency is given by the following equation:

$$F_{DDS} = F_{CLK} \times N_{FRQ} / 2^{32}$$

where  $F_{DDS}$  is the DDS output frequency,  $F_{CLK}$  is the DDS clock frequency and  $N_{FRQ}$  is the value programmed into the DDS chip's Frequency Register.


The resultant frequency increment is given by

$$\begin{aligned} F_{CLK} / 2^{32} &= 25 \text{ MHz} / 2^{32} \\ &= 5.821 \text{ millihertz} \end{aligned}$$

For the output frequency range of 0.2 - 0.4 MHz, the highest sidebands observed were less than  $-75$  dBc. The output of the DDS is lowpass filtered to remove the alias components due to sampling by the reference clock, and DC offset is set to 1.2 V as required later by the quadrature modulator.

*Phase-splitter and single-sideband (SSB) mixer* — The SSB mixer is formed with a phase splitter along with a quadrature modulator. The phase splitter contains two branches of all-pass networks that create a phase difference of 90 degrees over the DDS frequency range (Figure 2). The design of such phase splitters is described by Willams and Teylor [7]. Following the procedures from this reference, a 4-section network is selected to provide a quadrature error of 1.31 degree peak over the upper to lower frequency ratio of 11.47. The Frequency Scaling Factor (FSF) is given by
 
$$\begin{aligned} \text{FSF} &= 2\pi \times (F_{lower} \times F_{upper})^{1/2} \\ &= 2\pi \times [(0.2 \times 0.4) \times 10^6]^{1/2} \\ &= 7.10 \times 10^6 \text{ rad/s} \end{aligned}$$



▲ Figure 3. SSB mixer output spectrum.

The resistor values are computed by picking  $C = 1000$  pF and substituting in the formula

$$R_{xx} = 1 / (\alpha_{xx} \times \text{FSF} \times C)$$

where  $R_{xx}$  are the resistor values for the appropriate sections and  $\alpha_{xx}$  are the normalized pole values.

Section	$\alpha_N$	$\alpha_P$	$R_N$	$R_P$
1	5.9939	1.5027	102	402
2	0.5055	0.1280	1.21k	4.75k

The DC reference level of the phase splitter is set to 1.16 V using the DDS's on-chip reference to match that of the filtered DDS output. An additional inverting amplifier provides the required complimentary base-


band signals for the quadrature modulator that follows. The phase noise of the DDS signal at the phase splitter outputs is measured to be  $-116$  dBc/Hz at 10 kHz offset.

The quadrature modulator used is the AD8346 from Analog Devices [8], which can operate through the frequency range of 0.8 - 2.5 GHz. The baseband signals from the phase splitter are modulated onto the LO signal coming from the VCO. The desired lower sideband (LSB) output at the difference frequency is sent to the fractional-N PLL synthesizer chip. Also present in this output are the LO leakage at the VCO frequency and the unwanted sideband (USB) at the sum of the VCO and DDS frequencies, along with other intermodulation products. Figure 3 is the modulator's output spectrum, showing the LO leakage and USB at around 35 dB below the desired LSB signal. These unwanted signals will ultimately show up as additional tones modulating the VCO, and must be rejected by the loop filter.

**Fractional-N PLL** — The National Semiconductor LMX2350 2.5 GHz single-chip fractional-N PLL synthesizer has been selected for its flexibility and availability [9]. There are two synthesizer on the same chip,

though the 550 MHz IF synthesizer section is not used in this project. The LMX2350 contains registers to store values for the various reference and variable frequency dividers.

 **Coarse tuning** — A digital-to-analog converter (DAC), Analog Devices' DAC8512 [10], is used to set the coarse tuning voltage for the VCO. The 0 - 4 V output



▲ **Figure 4. Loop filter and coarse tuning circuit schematic.**

## Author Guidelines for Articles in Applied Microwave & Wireless

Applied Microwave & Wireless is here to help you present your work to the tens of thousands of engineers who are our readers. We do not require our authors to write in a precisely-defined format!

After sending a proposal to our editors and receiving its acceptance, you only need to address a few important matters as you prepare a finished manuscript:

- Present the material clearly and completely, but without being overly academic.
- Use correct spelling and grammar, and have someone you know proofread the paper.
- Provide graphs, charts and photos in a high-quality electronic form, or in sharp printouts
- Even if you e-mail or send the material to us on disk, also provide a printed copy, especially when the article contains several equations.
- There is no need to make it look like our magazine pages! That's our job.

Questions on the content and format can always be addressed to the Publisher or Managing Editor, or you may contact our Art Director for guidance on acceptable files for the graphics.

from the DAC is low-pass filtered, offset, amplified and heavily filtered again to cover the 2 - 22 V tuning voltage range as shown in Figure 4. The PLL will only need to correct for a small frequency error of the order of  $\pm 5$  MHz, thus the required tuning sensitivity is lowered along with its noise implications for the PLL. However, it still takes some very careful design and layout to minimize the amount of hum and unwanted signals presented to the VCO's tuning input.

*Loop filter design* — The loop bandwidth (LBW) of the PLL is chosen to optimize the phase noise performance of the loop. The multiplied reference noise is computed from

$$L(f) = 20 \times \log(N_{div}) + N_D$$

where  $N_{div}$  is the divide ratio in the PLL, and  $N_D$  is the noise floor of the PLL chip, assumed to be  $-160$  dBc/Hz (unconfirmed).

The contribution by the crystal reference is assumed to be negligible after being divided by the Reference Divider. With  $N_{div}$  varying from 1200 to 2400,  $L(f)$  lies between  $-98$  to  $-92$  dBc/Hz accordingly. With  $N_{div} = 1200$ , the VCO's phase noise will be equal to that of the multiplied reference at an offset frequency of 8 kHz. If the loop bandwidth is set also to the same frequency, then the resultant phase noise of the PLL will track that of the reference for offset frequencies below 8 kHz and that of the VCO above 8 kHz, getting the best of both worlds.

The VCO The procedure for designing the loop filter for a phase-locked loop can be found in many texts, such as Gardner [1]. The loop gain is given by


$$LG(s) = K_P \times K_V \times H(s) / (s \times N_{div})$$

where  $K_P$  is the phase detection constant,  $K_V$  the VCO tuning sensitivity, and  $H(s)$  is the transfer function of the loop filter.

In this case the pole of the loop filter (formed by  $R_5$  and  $C_2$ ) and the zero of the loop filter (formed by  $R_z$  and  $C_z$ ), are selected to obtain a frequency response where the loop gain crosses the unity line at 8 kHz and at a

Source	Frequency Offset	Level	Comment
DDS	anywhere	$\sim -72$ dBc	Unfilterable
Phase Detector Reference	1 MHz	$\sim -70$ dBc	Isolation limited
SSB Mixer (LO & USB)	0.2-0.8 MHz	$\sim -50$ dBc	Isolation + Filter
Crystal Oscillator	25 MHz	$\sim -50$ dBc	Isolation limited

 ▲ **Table 1. A list of the sources that contribute to spurious sidebands.**



▲ **Figure 5. Loop gain and loop filter response.**

slope of  $-20$  dB/decade to ensure stability.

The loop filter output is then resistively summed with the coarse tuning voltage. The overall response of the loop gain and that of the loop filter (from the charge pump output to the VCO's tuning input) is shown in Figure 5.

*Programming interface* — Programming of the PLL's frequency is through a PC parallel port into the serial interfaces of the different sections. Since each of the three devices, DDS, DAC and PLL, uses a three wire serial interface, the Clock and Data lines are shared, and each

Latch Enable input is driven by a separate bit from the PC's parallel port.

## Performance analysis

*Phase noise* — At offsets less than the PLL's loop bandwidth, phase

noise is dominated by the reference divider noise floor ( $\sim -160$  dBc) +  $20 \log(N_{div})$ , where  $N_{div}$  is the divide ratio (1199.6 - 2399.8), which gives  $-98$  to  $-92$  dBc/Hz. Phase noise outside the loop bandwidth is set by the VCO and its tuning circuitry.

The phase noise of a breadboard prototype version of the frequency synthesizer is shown in Figure 6. With  $-76$  dBc/Hz at 10 kHz offset, the synthesizer is far from obtaining its potential of  $-92$  to  $-98$  dBc/Hz level. Most of this excess noise can be attributed to inadequate power supply and voltage reference conditioning, so that broadband noise is coupled into the VCO. (Frequency synthesizer designers are known to use the largest quantity of tantalum capacitors per unit area on the printed circuit, in addition to the heavy metal armor around the circuitry). At an offset of 100 kHz, the phase noise finally comes back down to  $-116$  dBc/Hz, which is close to the performance of the VCO alone.

*Spurious sideband levels* — There are several contributors to spurious sidebands. The sources and the results measured on the prototype breadboard circuit are listed in Table 1.


The DDS generates low level spurious sidebands all over its spectrum. Those that fall inside or close to the loop bandwidth cannot be filtered off. Fortunately, by running the DDS output at a small fraction of its clock frequency, these spurious signals are kept to a low level. The Phase Detector Reference sideband is trapped in the loop filter, and only shows up due to the limited isolation on the breadboard. The SSB Mixer spurs require a more careful design of the loop filter as they fall closer to the loop bandwidth and they suffer from the lack of isolation due to the construction of the breadboard. The 25 MHz crystal reference is present all over the breadboard and, like the two previous sources, it needs a better layout to provide the necessary isolation.

*Frequency settling time* — Frequency settling time is mostly limited by the requirement to adequately filter the SSB mixer spurs and fractional-N jitter with offsets from 0.2 to 0.8 MHz, and also by the fact that the coarse tuning output needs to be heavily filtered. The performance on the breadboard was severely hampered as the coarse tuning path does not have any

means to reduce the filtering during a frequency change.
 
## Conclusion

The microwave synthesizer presented above demonstrates the simplicity of the design. The whole synthesizer can be built from readily available components, and the resultant printed circuit board can fit in the palm of a hand. In order to reach



▲ **Figure 6. Synthesizer phase noise plot.**

the full potential in phase noise, spurious level and switching performance, greater attention must be given to the details of a careful layout and power supply conditioning. ■

## References

1. Floyd M. Gardner, *Phaselock Techniques*, 2nd ed., John Wiley & Sons, 1979.
2. William F. Egan, *Frequency Synthesis by Phaselock*, John Wiley & Sons, 1981.
3. Vadim Manassewitsch, *Frequency Synthesizers*, John Wiley & Sons, 1987.
4. Ulrich Rhode, *Digital PLL Frequency Synthesizers: Theory and Design*, Prentice Hall, 1983.
5. VCO V6009001 data sheet, Z-Communications, Inc.
6. AD9832 data sheet, Analog Devices, Inc.
7. Arthur B. Williams and Fred J. Taylor, *Electronic Filter Design Handbook*, 3rd ed., McGraw Hill, 1995.
8. AD8346 data sheet, Analog Devices, Inc.
9. LMX2350 data sheet, National Semiconductor.
10. DAC8512 data sheet, Analog Devices, Inc.

## Author information

Benjamin Sam graduated from the Hong Kong Polytechnic in 1979 with the Higher Diploma in Electronics Engineering and received BS and MS degrees in Electrical Engineering from the University of Texas at Arlington in 1980 and 1982 respectively. He works at Analog Devices' Northwest Labs in Beaverton, OR, designing RFICs. He is the designer of the AD8346 Quadrature Modulator mentioned in this article. Previous experience includes developing RF test equipment at Wavetek RF Products and Tektronix as well as signal coverage analysis for the Receptor™ Pager-watch program at AT&E Labs (now Seiko Communications). He can be reached by e-mail at [benjamin.sam@analog.com](mailto:benjamin.sam@analog.com)