

# Choosing the Right Diode for your AGC Detector

Here are the performance characteristics you should know for detector design


By **Raymond W. Waugh**  
Hewlett-Packard Company

**A**utomatic Gain Control (AGC) loops are used to control the gain or output power of amplifiers in a wide variety of applications. A typical circuit is shown in Figure 1.


In this circuit, a coupler (distributed transmission line as shown, or lumped element) couples off a small amount of power from the amplifier and feeds it to a Schottky diode detector. The detector produces a DC voltage proportional to the output power, which is then fed back to the amplifier's gain control circuit. Diode detectors of this type can be externally biased or self biased [1]. Let us first examine the self-biased detector.

The typical self-biased detector (sometimes referred to as "zero-biased") is shown in Figure 2. A diode is combined with a capacitor of sufficient size on the DC side to present a low impedance (compared to that of the diode), and a shunt 68 ohm resistor is placed on the RF side. This resistor serves two functions — it provides a good impedance match at the input to the detector circuit and furnishes a return path for the DC current generated in the diode. The circuit is completed with a DC load resistor of 1 kohm to 10 kohms.

In the lower half of Figure 2, the diode is replaced with its linear equivalent circuit, which can provide insight into the performance of the detector diode.  $L_p$  and  $C_p$  are package parasitics — little can be done to change their values. The diode chip itself can be represented by a three-element equivalent circuit, including  $R_s$  (parasitic series resistance),  $C_j$  (parasitic junction capacitance) and  $R_j$  (the junction resistance of the diode, where RF energy is converted to DC voltage). As frequency or junction capacitance increases, the junction resistance of the diode

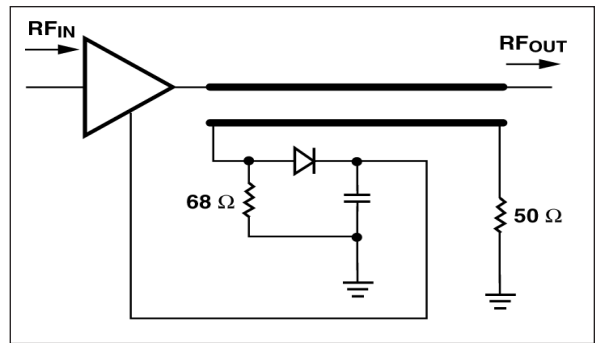


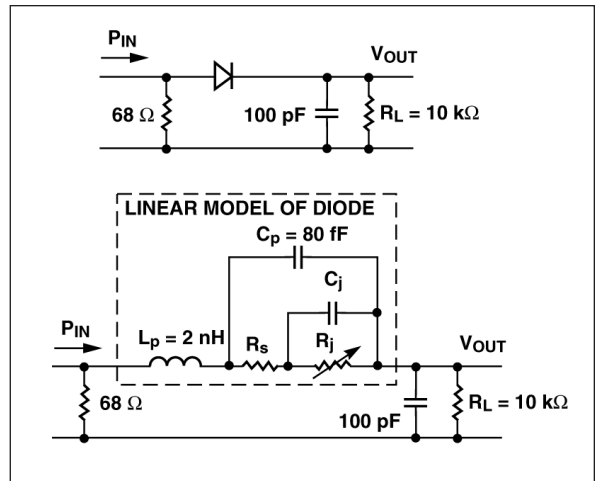▲ Figure 1. A typical AGC circuit using a Schottky diode detector.



▲ Figure 2. A typical self-biased or "zero biased" detector. Below the schematic is the linear equivalent circuit.

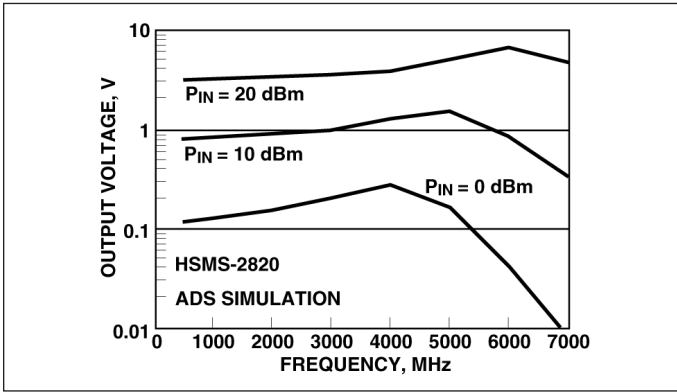will be shorted out and RF energy will be diverted to  $R_s$  where it is converted into heat. When this occurs, output voltage will fail.



▲ **Figure 3. Simulation of the HSMS-282x diode family showing the effect of the relatively large junction capacitance in high-frequency rolloff.**


This analysis becomes more complex because junction resistance in a self-biased detector is a variable. As input  $P_{in}$  increases,  $V_{out}$  will increase, and thus the magnitude of the current circulating through  $R_L$  will increase. As this current rises, the value of  $R_j$  will fall, diminishing the effect of junction capacitance. The best way in which to conduct the analysis is with a harmonic balance CAD program such as ADS [2].

Schottky diodes are available with a variety of characteristics, based upon the way in which they are fabricated. Diodes based upon p-type silicon feature very low barrier height, making excellent self-biased signal detectors ( $P_{in} < -20$  dBm). However, such devices have very low breakdown voltage, severely limiting the maximum value of  $P_{in}$ , and very high values of  $R_s$ . Diodes based upon n-type silicon offer lower values of series resistance, but their higher barrier height requires a higher value of  $P_{in}$  before they begin self-bias. Junction capacitance of the diode can be lowered by reducing the diameter of the Schottky junction, but this comes at the expense of lower yields, lower lot-to-lot consistency and higher cost.


A typical selection of Schottky detector diodes is shown in Table 1. This table provides the key SPICE parameters for the diodes. In addition to  $C_j$  and  $R_s$  (already defined), they are  $I_s$  (saturation current, an indicator of diode barrier height),  $V_{br}$  (breakdown voltage) and  $n$  (ideality factor). Also shown are ratings of diode cost and lot-to-lot consistency.

Simulations of AGC detectors of the type illustrated in Figure 2 were conducted on ADS, for values of input power ( $P_{in}$ ) of 0, 10 and 20 dBm and frequencies from 500 MHz to 7 GHz. The results of these analyses are shown in Figures 3, 4 and 5.

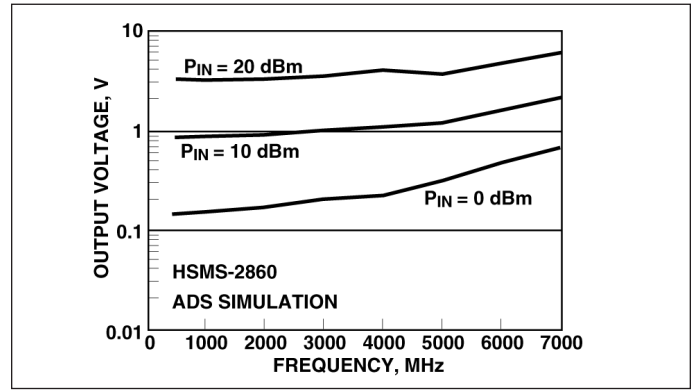In Figure 3, the effect of the relatively large junction capacitance of the HSMS-282x family of diodes is seen in the rolloff of output voltage at high frequencies, particularly at lower values of input power where junction resistance is higher. This low cost and consistent diode



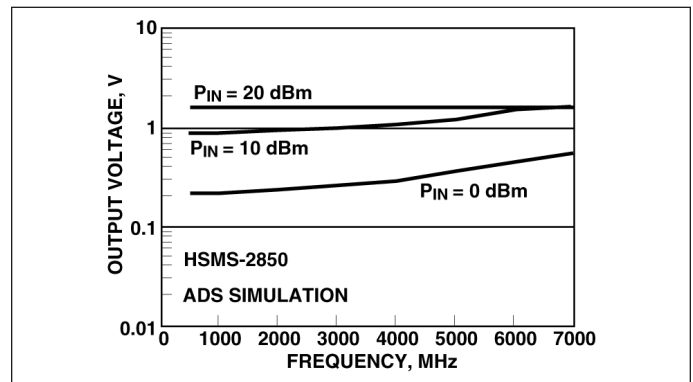▲ **Figure 4. Simulation of the HSMS-286x diode family showing improved performance above 4 GHz.**



▲ **Figure 5. Simulation of the HSMS-285x diode family of small-signal zero-bias detectors. Such p-type low-barrier diodes are characterized by series resistance and low breakdown voltage, causing the diode to saturate.**

makes an excellent AGC detector at frequencies below 4 GHz, but ought not to be used at higher frequencies.

The HSMS-286x family of microwave detector diodes offers superior performance at frequencies over 4 GHz, as can be seen in Figure 4. However, the higher cost and lot-to-lot variation of this part makes it a poor choice for frequencies below 4 GHz.

Figure 5 presents the results of the simulation for the HSMS-285x family of small signal zero-bias detectors. At first glance, it appears that its performance in an AGC circuit matches that of the n-type HSMS-286x family. However, p-type low-barrier diodes are characterized by high series resistance and low breakdown voltage. While these characteristics cause no problems in the performance of a small signal detector, they lead to severe performance limitations in large-signal AGC detectors. As shown in Figure 5, low breakdown voltage causes the diode output to saturate, especially at frequencies above 4 GHz. P-type diodes such as the HSMS-285x family should never be used for AGC detector applications (see Table 2).

Device	HSMS-282x	HSMS-286x	HSMS-285x
material	n-type	n-type	p-type
Cj, pF	0.65	0.12	0.13
Rs, $\Omega$	7.8	9.0	35.0
Is, A	1.5E-8	5E-8	3E-6
Vbr, V	26.7	7.0	4.8
n	1.067	1.080	1.100
cost	low	moderate	moderate
consistency	very high	high	low

▲ **Table 1. Key diode SPICE parameters and indication of relative cost and degree of lot-to-lot consistency.**

In summary, low-cost diodes such as the HSMS-282x family make excellent self-biased AGC detectors at frequencies below 4 GHz, while the HSMS-286x family of microwave detector diodes would be a better choice at frequencies above that limit. P-type low-barrier diodes are never used in applications where the input power is higher than -20 dBm. ■


## References


1. Raymond W. Waugh, "Designing Large-Signal Detectors for Handsets and Base Stations," *Wireless Systems Design*, Volume 2, Number 7, July 1997.
2. *Advanced Design System*, Hewlett-Packard Company.
 
## Author information

Raymond W. Waugh is diode applications engineer for the Wireless Semiconductor Division of Hewlett-Packard Company. He is a Senior Member of the IEEE, a member of the Microwave Theory and Techniques Society, and is on the editorial board for *IEEE Transactions*. He is also a member of SAE.

Waugh obtained his BSEE degree from the University of Michigan in 1962 and his MSEE from UCLA in 1968. He has written or co-written approximately 20 papers, and has conducted diode design seminars in Europe, Asia and the United States. He may be contacted at: ray\_waugh@hp.com








## 2000 IEEE-APS CONFERENCE ON ANTENNAS AND PROPAGATION FOR WIRELESS COMMUNICATIONS

*Waltham, MA — November 6-8, 2000*

Plan to attend the 2000 Conference on Antennas  
and Propagation for Wireless Communications!

As Co-chairs of the 2000 IEEE-APS Conference on Antennas and Propagation for Wireless Communications, and on behalf of the Organizing Committee, we would like to invite you to attend the conference, to be held November 6-8, 2000, in Waltham, Massachusetts. It is an exciting time to be working in the field of antennas and propagation, due in no small part to the explosive growth of wireless communications.

Deployment of cellular telephone equipment, PCS, and wireless local loop service is rapidly evolving worldwide. Commercial application of systems which were originally developed for defense applications, such as GPS and spread spectrum techniques, are adding new capabilities and improvements in performance to consumer applications. Technical sessions will cover topics relevant to real-world problems in wireless antennas and propagation, and each session will begin with an overview presented by an expert in the field. And because this conference is small and focused, you will have the opportunity to discuss these developments with the speakers and other conference attendees. In addition, we will be hosting an exhibit hall for companies involved with wireless products, and will be conducting several short courses specifically on topics in wireless antennas and propagation.

We think this will be an exciting conference, and look forward to seeing you there!

*Professor Christos Christodoulou and Dr. Tuli Herscovici*  
Conference Co-Chairmen

For more details, call the conference office at **781-890-5290**, e-mail to [bostonieee@aol.com](mailto:bostonieee@aol.com) or visit the conference web site at <http://www.eece.unm.edu/apwc2000/> where you can review the technical program and download the registration form.